

# **ECE/ENGRD 2100**

## Introduction to Circuits for ECE

### Lecture 38


#### Mutual Inductance and Transformers

# Announcements

---

- Recommended Reading:
  - Textbook Chapter 6.4-6.5 and Chapter 9.10-9.11
- Upcoming due dates:
  - Homework 5 due by 11:59 pm on Monday April 29, 2019
  - Prelab 6 due by 11:59 pm on Monday April 29, 2019
  - Lab report 6 due by 11:59 pm on Friday May 3, 2019
  - Homework 6 due by 11:59 pm on Tuesday May 7, 2019

# Inductance (Self-Inductance)

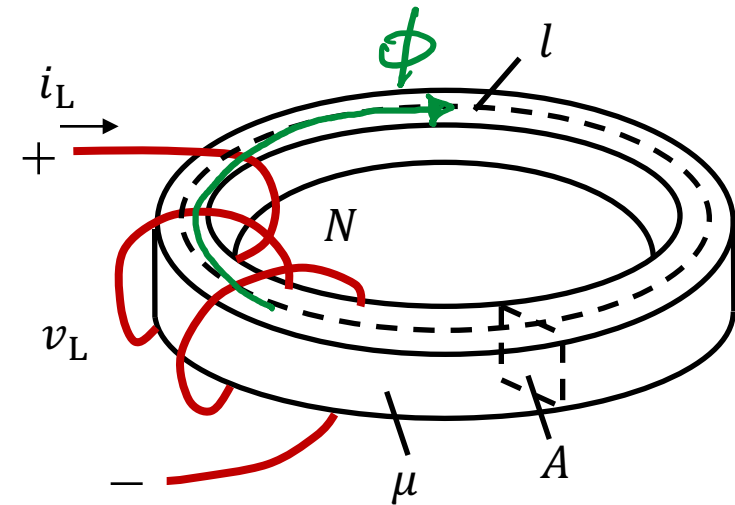


Faraday's Law:  $v_L = \frac{d\lambda_L}{dt}$

$$\lambda_L = N\Phi = N(BA) = N(\mu H)A = \mu N \left( \frac{Ni_L}{l} \right) A$$

→  $\lambda_L = \frac{\mu AN^2 i_L}{l}$  ( $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$ )

$$\lambda_L = Li_L$$

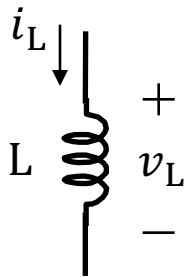
$$L \equiv \frac{d\lambda_L}{di_L} = \frac{\mu AN^2}{l} = \mathcal{P} N^2$$



$$v_L = L \frac{di_L}{dt}$$
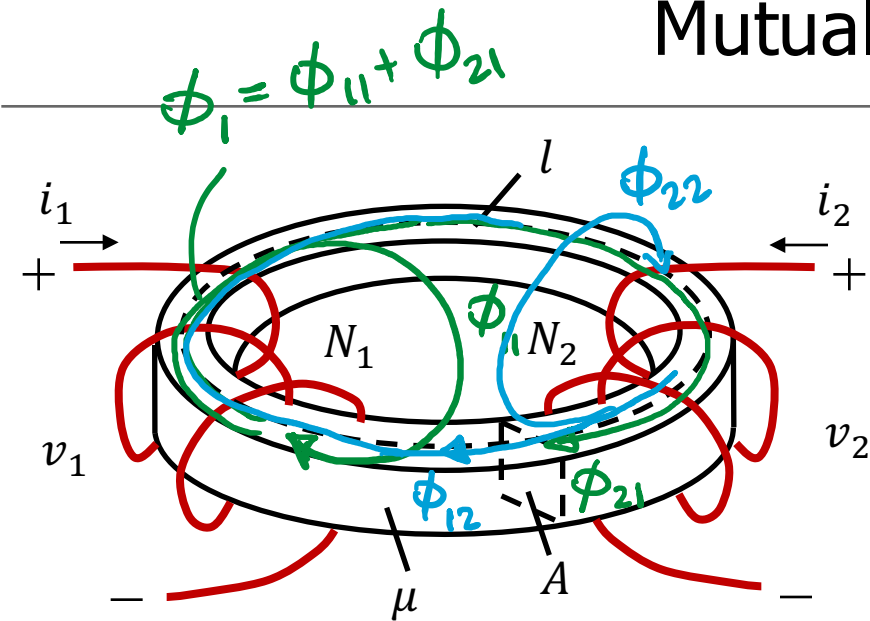
# Mutual Inductance

- Use right-hand-rule to determine direction of flux




*self-inductance*


*mutual inductance*

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$


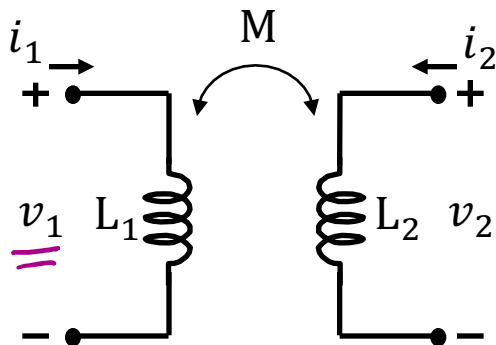
$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



# Dot Convention

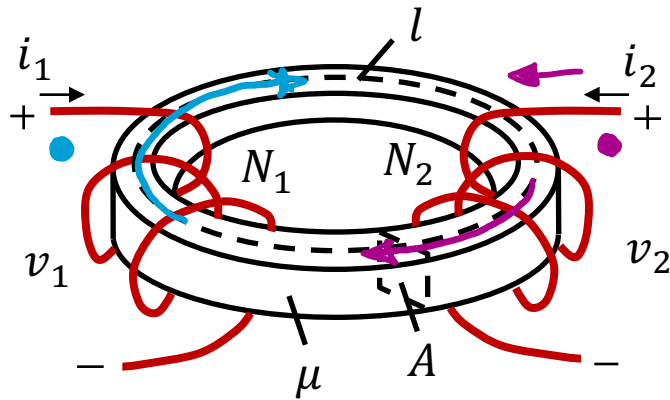

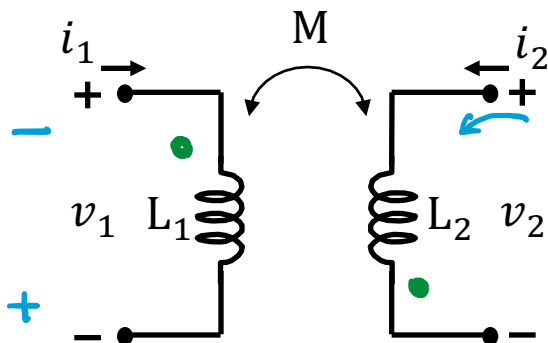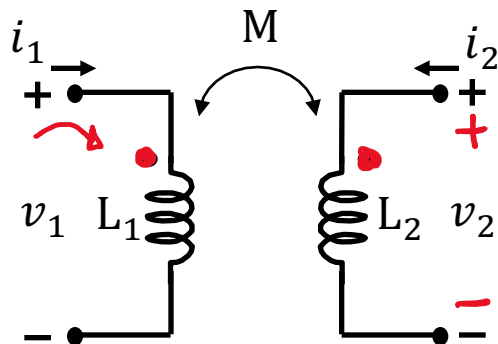- Currents into the dot generate flux inside the coupled coils in the same direction
- When the reference direction for a current enters the dotted terminal of a coil, the reference polarity of the voltage that it induces in the other coil is positive at its dotted terminal




$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$v_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$
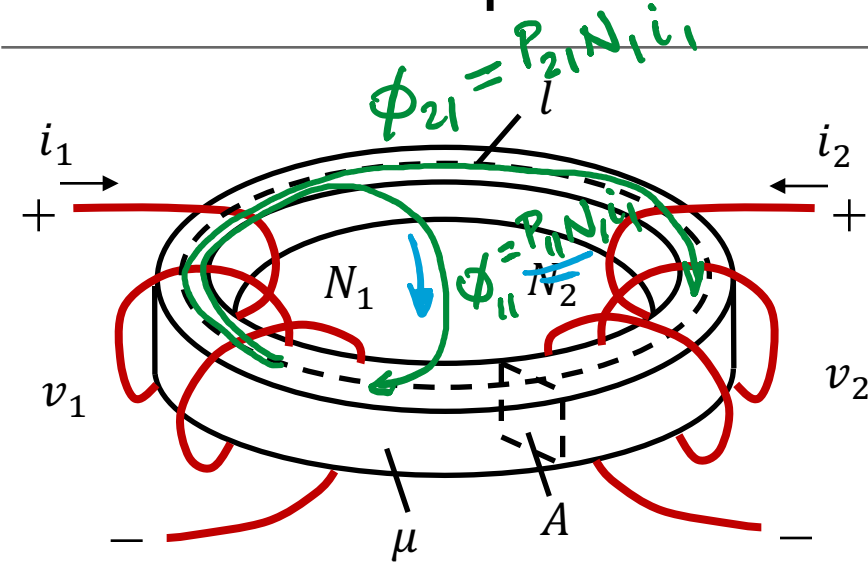
# Relationship Between Mutual and Self Inductances



$$\underline{L_1} = \frac{d\lambda_1}{di_1} = \underline{P_1 N_1^2} = \underline{(P_{11} + P_{12}) N_1^2}$$

$$\underline{L_2} = \frac{d\lambda_2}{di_2} = P_2 N_2^2 = \underline{(P_{22} + P_{21}) N_2^2}$$

$$\underline{M} = \frac{d\lambda_2}{di_1} = \frac{d\lambda_1}{di_2} = \underline{P_{21} N_2 N_1} = \underline{P_{12} N_1 N_2}$$

$P_{21} = P_{12}$

$$M_{21} = \frac{\lambda_{21}}{i_1} = \frac{N_2 P_{21} N_1 i_1}{i_1} = P_{21} N_2 N_1 = P_{12} N_1 N_2 = M_{12} \equiv M$$



$$\underline{L_1 L_2} = \underline{P_1 N_1^2} \underline{P_2 N_2^2} = \underline{(P_{11} + P_{12}) (P_{22} + P_{21}) N_1^2 N_2^2} = P_{12} P_{21} \left(1 + \frac{P_{11}}{P_{21}}\right) \left(1 + \frac{P_{22}}{P_{12}}\right) N_1^2 N_2^2$$

$$L_1 L_2 = \underbrace{(P_{12} N_1 N_2)}_M \underbrace{(P_{21} N_1 N_2)}_M \left(1 + \frac{P_{11}}{P_{21}}\right) \left(1 + \frac{P_{22}}{P_{12}}\right)$$

$$M = \frac{1}{\sqrt{\left(1 + \frac{P_{11}}{P_{21}}\right) \left(1 + \frac{P_{22}}{P_{12}}\right)}} \sqrt{L_1 L_2} \equiv k \sqrt{L_1 L_2} \quad 0 \leq k \leq 1$$

Coupling Coefficient

# Ideal Transformer

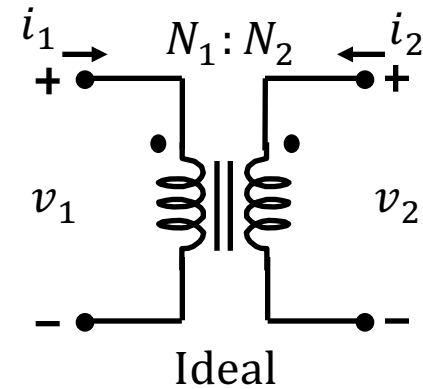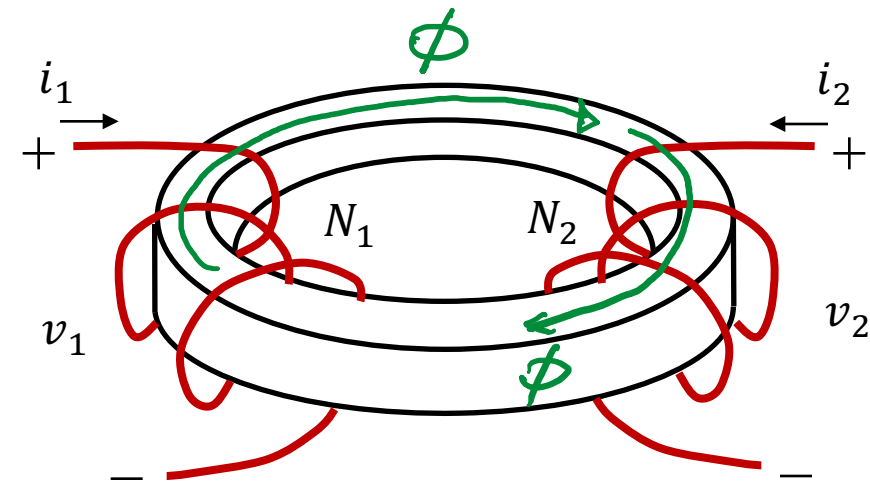

$$\left. \begin{aligned} v_1 &= \frac{d\lambda_1}{dt} = \frac{dN_1\phi}{dt} = N_1 \frac{d\phi}{dt} \\ v_2 &= \frac{d\lambda_2}{dt} = \frac{dN_2\phi}{dt} = N_2 \frac{d\phi}{dt} \end{aligned} \right\}$$


$$\frac{v_2}{v_1} = \frac{N_2 \frac{d\phi}{dt}}{N_1 \frac{d\phi}{dt}} = \frac{N_2}{N_1}$$

Lossless and stores no energy  $\Rightarrow P_1 = P_2 \Rightarrow v_1 i_1 = -v_2 i_2$

$$\Rightarrow \frac{i_2}{i_1} = -\frac{v_1}{v_2} = -\frac{N_1}{N_2}$$


$$\boxed{\frac{v_2}{v_1} = \frac{N_2}{N_1}} \quad \& \quad \boxed{\frac{i_2}{i_1} = -\frac{N_1}{N_2}}$$
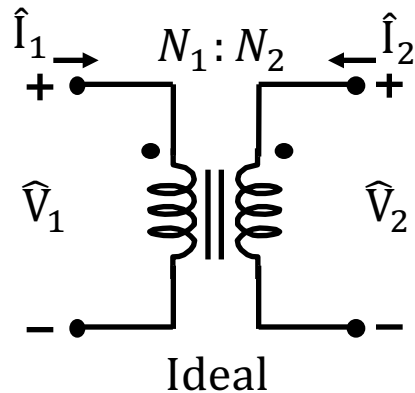
# Ideal Transformer – Impedance Transformation



$$\frac{\hat{V}_2}{\hat{V}_1} = \frac{N_2}{N_1}$$
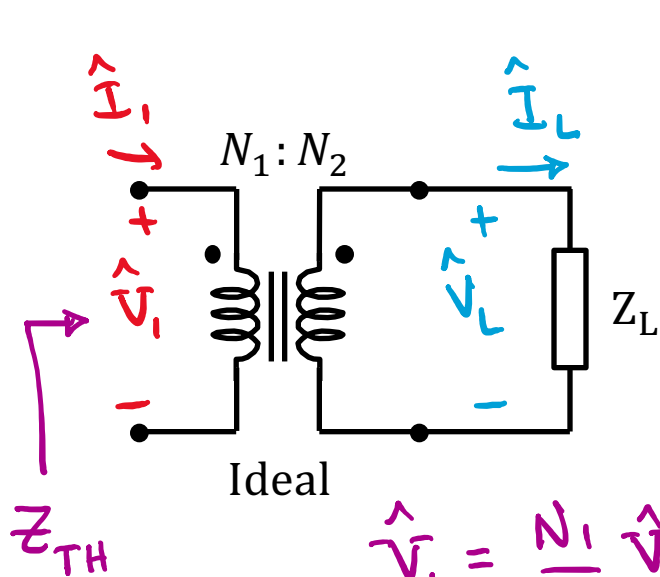
$$\frac{\hat{I}_2}{\hat{I}_1} = -\frac{N_1}{N_2}$$



$$Z_L = \frac{\hat{V}_L}{\hat{I}_L}$$

$$Z_{TH} \equiv \frac{\hat{V}_1}{\hat{I}_1} = \frac{N_1}{N_2} \hat{V}_L \cdot \frac{N_1}{N_2} \frac{1}{\hat{I}_L}$$




$$\begin{aligned} \hat{V}_1 &= \frac{N_1}{N_2} \hat{V}_L \\ \hat{I}_1 &= \frac{N_2}{N_1} \hat{I}_L \end{aligned}$$

$$\Rightarrow Z_{TH} = \left( \frac{N_1}{N_2} \right)^2 \frac{\hat{V}_L}{\hat{I}_L}$$


$$\Rightarrow Z_{TH} = \left( \frac{N_1}{N_2} \right)^2 Z_L$$


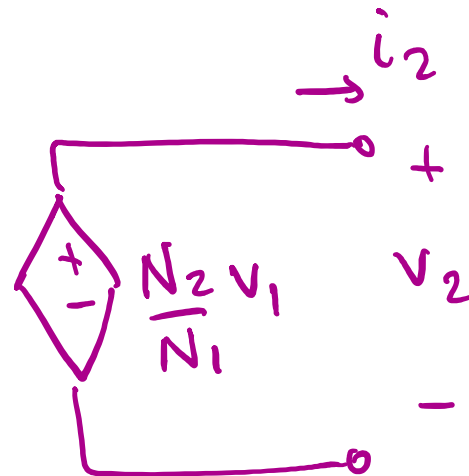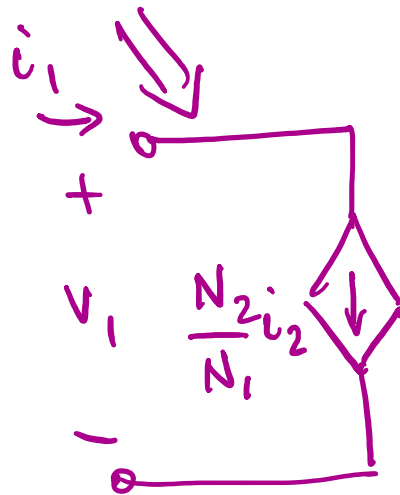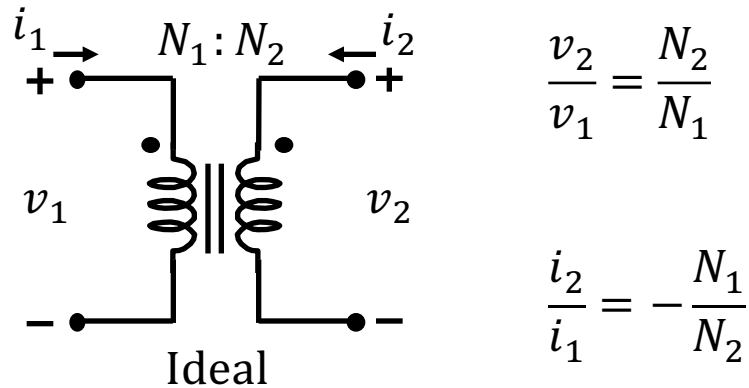
# Ideal Transformer – Dependent Source Model



# Non-Ideal Transformer Model

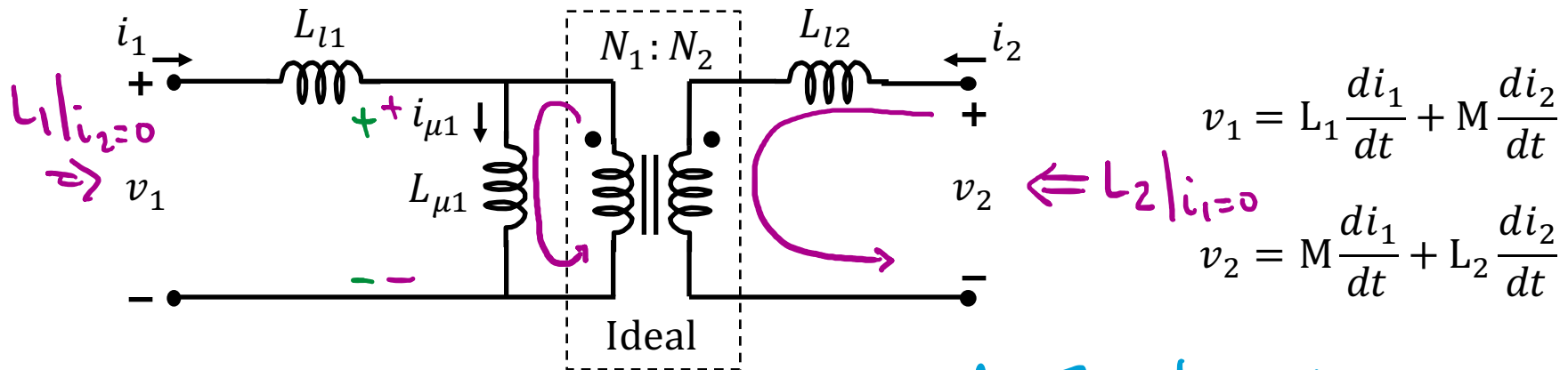

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

$$L_1 = L_{l1} + L_{\mu 1}$$

$$L_2 = L_{l2} + \left(\frac{N_2}{N_1}\right)^2 L_{\mu 1}$$

$$M = \frac{N_2}{N_1} L_{\mu 1}$$

Ideal Transformer

$$\left. \begin{array}{l} L_{l1} = 0 \\ L_{l2} = 0 \end{array} \right\} \Rightarrow \begin{array}{l} L_1 = L_{\mu 1} \\ L_2 = \left(\frac{N_2}{N_1}\right)^2 L_{\mu 1} \end{array}$$

$$M = \frac{N_2}{N_1} L_{\mu 1}$$

$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{\frac{N_2}{N_1} L_{\mu 1}}{\sqrt{L_{\mu 1} \left(\frac{N_2}{N_1}\right)^2 L_{\mu 1}}} = 1$$

$L_{\mu 1} \rightarrow \infty$