

ECE/ENGRD 2100

Introduction to Circuits for ECE

Lecture 39

Power in AC Systems

Announcements

- Recommended Reading:
 - Textbook Chapter 10
- Upcoming due dates:
 - Lab report 6 due by 11:59 pm on Friday May 3, 2019
 - Homework 6 due by 11:59 pm on Tuesday May 7, 2019

Power System


$$v_A(t) = V \cos(\omega t)$$

$$v_B(t) = V \cos(\omega t + 120^\circ)$$


$$v_C(t) = V \cos(\omega t - 120^\circ)$$

$$\omega = 2\pi f$$

$$f = 60 \text{ Hz}$$

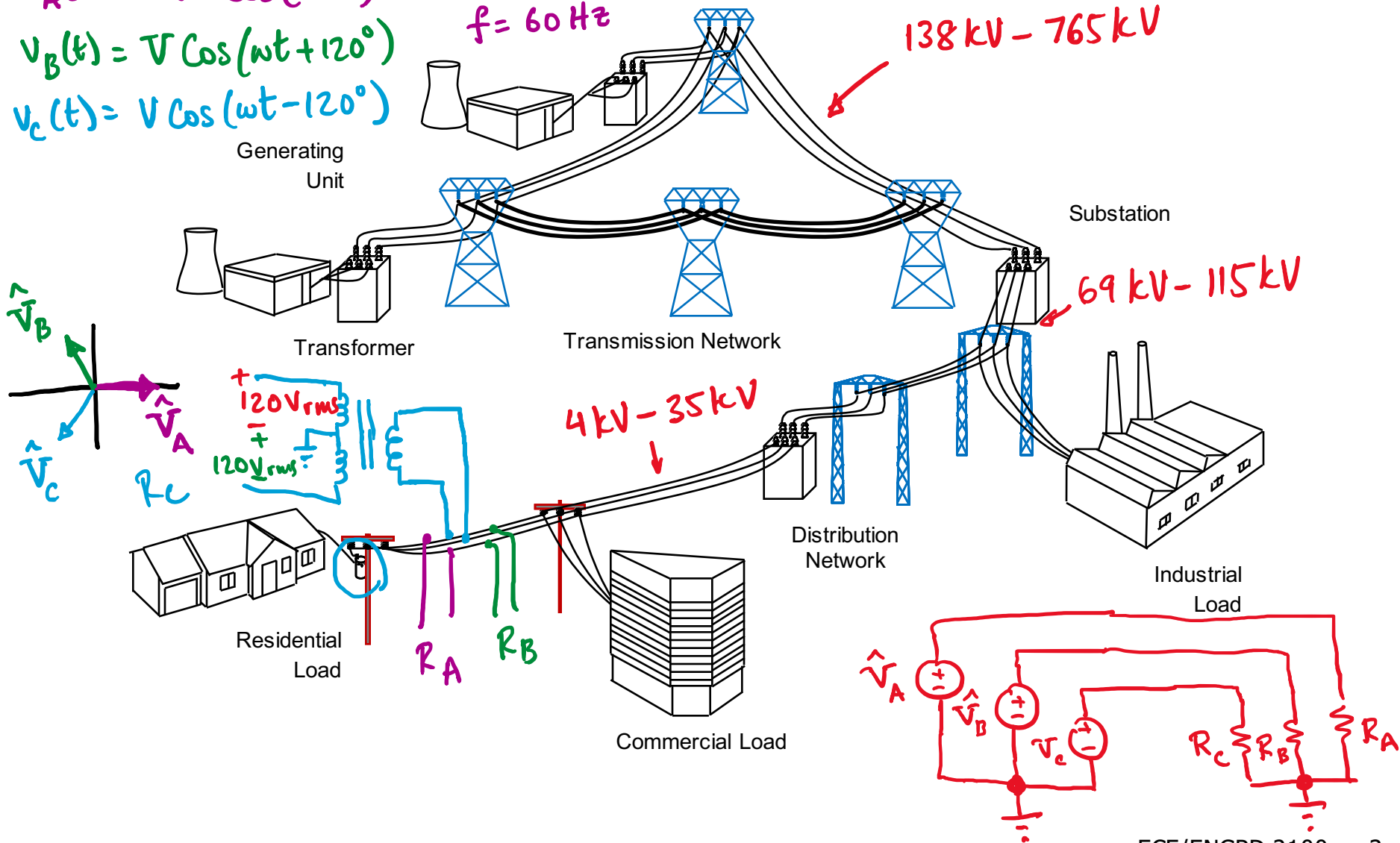

Instantaneous Power and Average Power

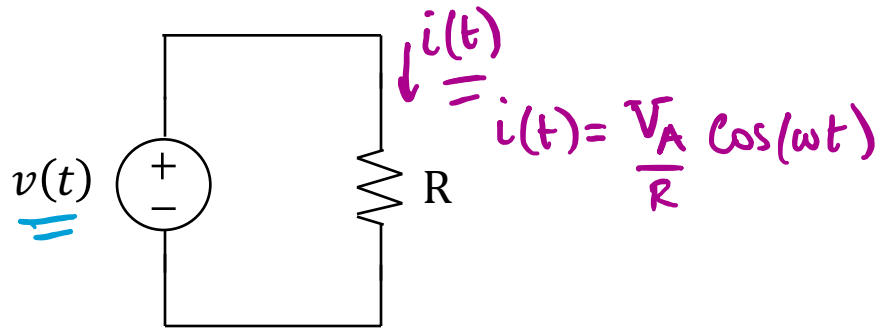

$$v(t) = V_A \cos(\omega t)$$

$$p(t) = v(t)i(t) = \frac{V_A^2}{R} \cos^2(\omega t)$$

$$p(t) = \frac{V_A^2}{2R} [1 + \cos(2\omega t)]$$

← Instantaneous Power


$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} \cdot \frac{V_A^2}{R}$$

Average Power (also called "Real Power" & "Active Power")


Trigonometric Identity

$$\cos(2\theta) = 2 \cos^2(\theta) - 1$$
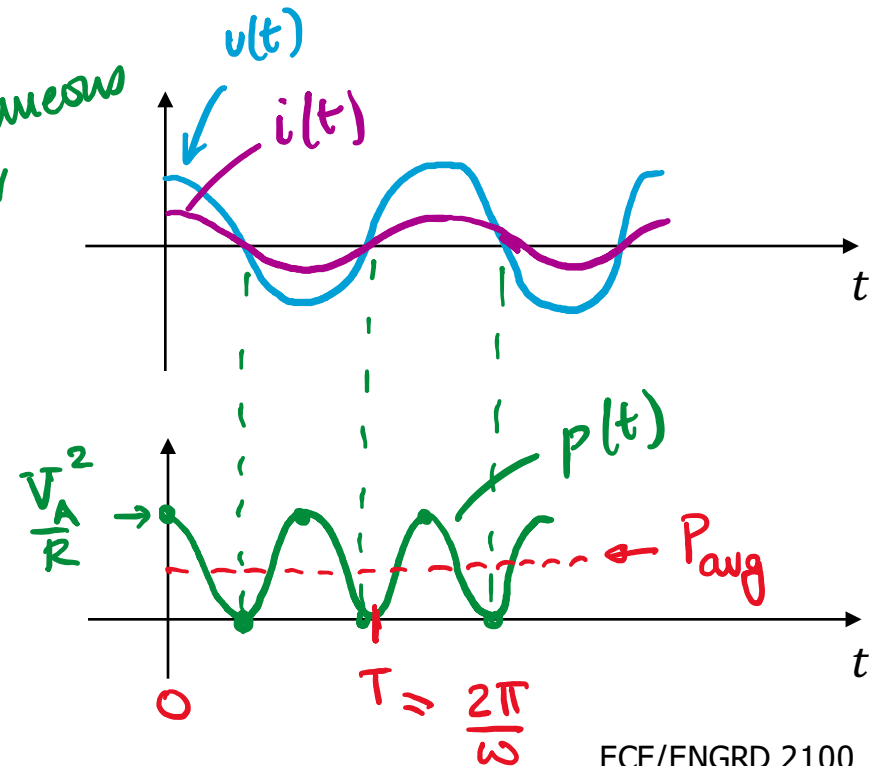
$$\Rightarrow \cos^2(\omega t) = \frac{1 + \cos(2\omega t)}{2}$$



Root Mean Square (RMS) Value

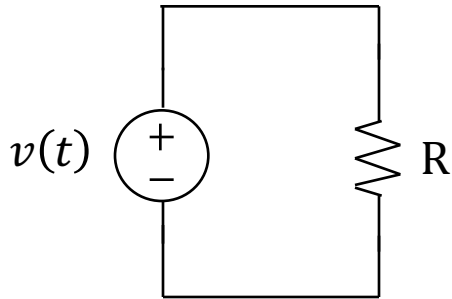

$$v(t) = V_A \cos(\omega t)$$

The RMS value of a time varying voltage or current is the equivalent constant (i.e., dc) value that delivers the same amount of average power to a resistive load

Delivers same average power to resistive load as 120 V dc


$$V_{rms} = 120 V_{rms} \rightarrow V = \sqrt{2} \cdot 120 \approx 170 V$$

$$V_{rms} = \frac{V}{\sqrt{2}}$$

$$v(t) = V \cos(\omega t)$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_t^{t+T} v(t)^2 dt}$$

Power Delivered to a Capacitive Load

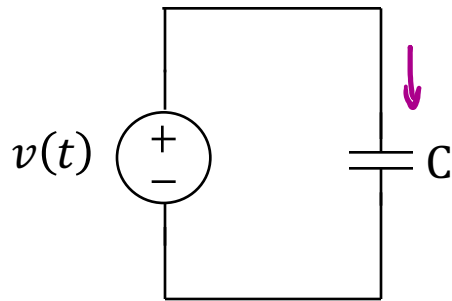

$$i_c(t) = C \frac{dv_c}{dt}$$
$$= -V_A \omega C \sin(\omega t)$$

$$v(t) = V_A \cos(\omega t)$$


$$p(t) = v(t)i(t) = -V_A^2 \omega C \cos(\omega t) \sin(\omega t)$$

$$p(t) = -\frac{V_A^2 \omega C}{2} \sin(2\omega t)$$


$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt = 0$$

Trigonometric Identity
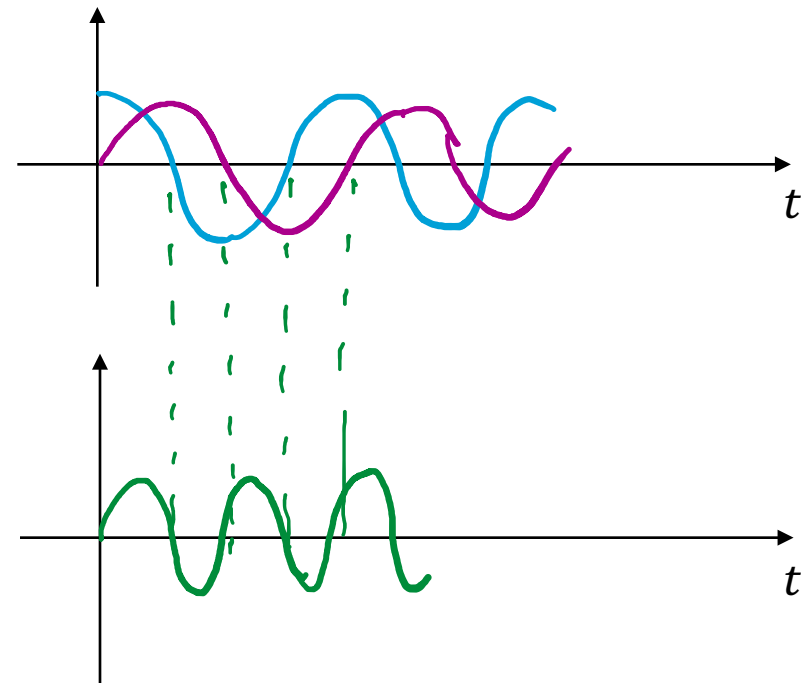
$$\sin(2\theta) = 2 \sin(\theta) \cos(\theta)$$




Power Delivered to an Inductive Load

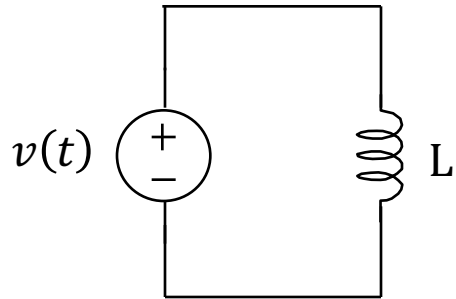


$$v(t) = V_A \cos(\omega t)$$

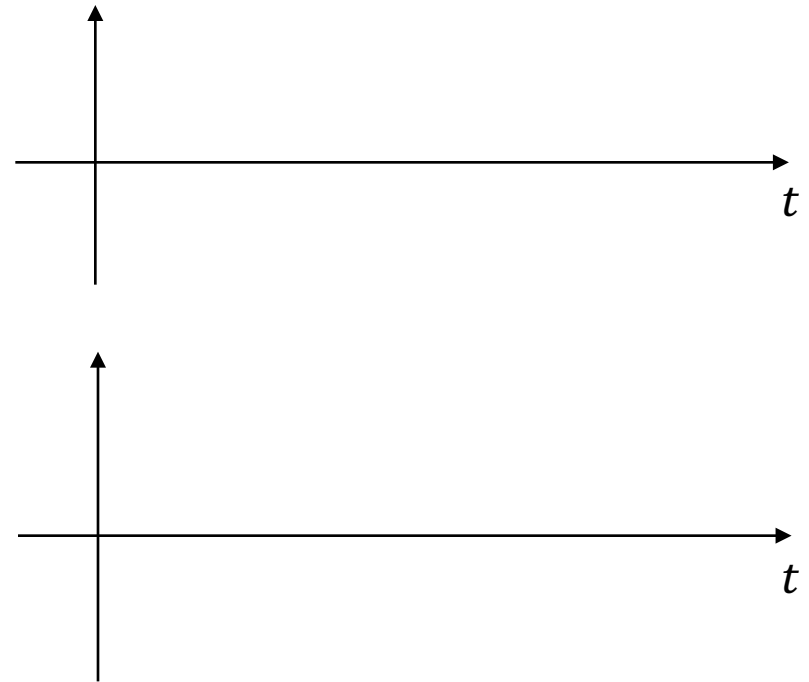
$$P_{avg} = \frac{1}{T} \int p(t) dt = 0$$



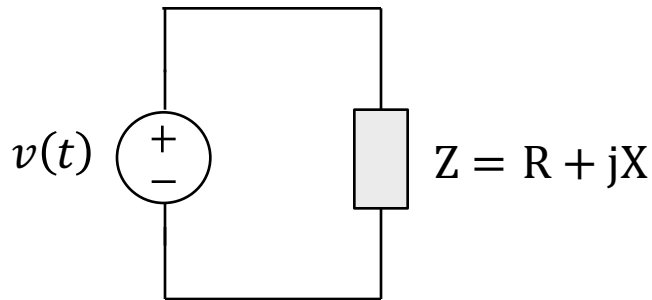Power Delivered to an Arbitrary R-L-C Load



$$v(t) = V_A \cos(\omega t)$$

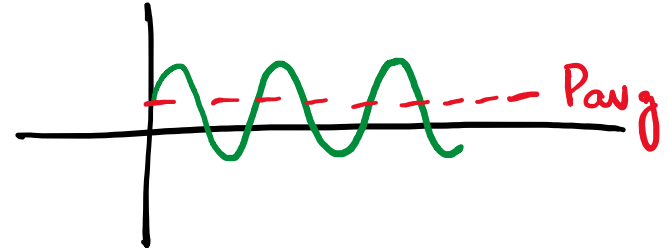

$$v(t) = V \cos(\omega t)$$

$$i(t) = I \cos(\omega t + \phi)$$

$$P_{avg} = VI \cos(\phi)$$

General Method


Find either the magnitude of the voltage across the resistor V_R , or the magnitude of the current through the resistor I_R , and then apply:

$$P_R = \frac{1}{2} \frac{V_R^2}{R}$$

$$\text{or } P_R = \frac{1}{2} I_R^2 R$$

$$\text{Reactive Power} = VI \sin(\phi)$$

Average Power Example

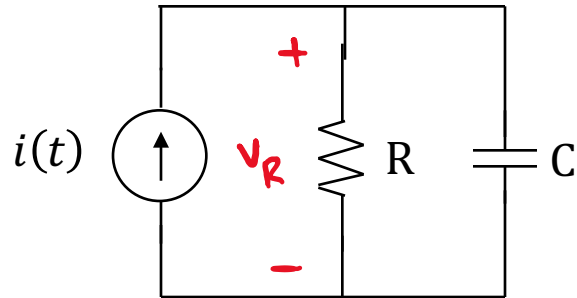


Determine average power delivered to the R-C load

$$P_{avg} = \frac{1}{2} \frac{\hat{V}_R^2}{R}$$

$$i(t) = I_A \cos(\omega t)$$
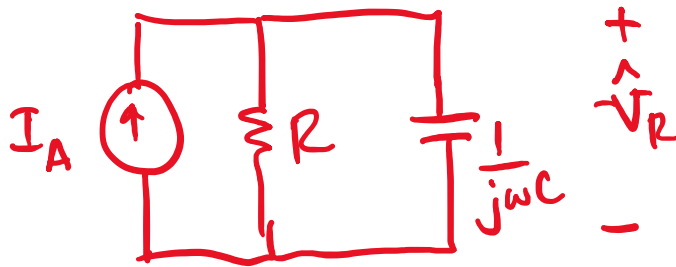
$$v_R = \hat{V}_R \cos(\omega t + \phi)$$




$$\hat{V}_R = [R \parallel (1/j\omega C)] I_A$$

Average Power in Terms of Phasors

$$P_{\text{avg}} = \frac{1}{2} \text{Re}\{\hat{V}\hat{I}^*\} = \frac{1}{2} \text{Re}\{\hat{V}^*\hat{I}\}$$
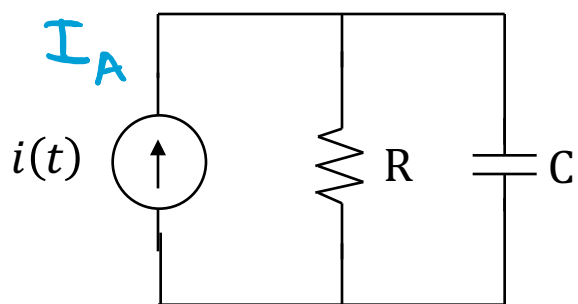
$$P_{\text{avg}} = \frac{1}{2} \text{Re}\{\hat{V}_R e^{-j\phi_R} I_A\}$$



$$\hat{V}_R = V_R e^{j\phi_R}$$

$$i(t) = I_A \cos(\omega t)$$