

ECE/ENGRD 2100

Introduction to Circuits for ECE

Lecture 4

Node Analysis


Announcements

- Recommended Reading:
 - Textbook Chapter ? 4
- Upcoming due dates:
 - Homework 1 due by 11:59 pm on Friday February 1, 2019
 - Lab report 1 due by 11:59 pm on Friday February 8, 2019

Circuit Analysis Techniques


- Brute force method of writing KVL, KCL and element constitutive relationships results in a large number of simultaneous equations to be solved
 - $2B$ equations have to be solved for $2B$ branch variables, where B is the number of branches/elements in the circuit
- Circuit simplification techniques/tricks do not always work *Review Voltage, Current divide*
- **Node Analysis** always works and requires fewer equations to be solved
 - Node analysis is also based on a combination of KVL, KCL and element constitutive relationships, but the analysis is organized in such a way that fewer equations have to be solved
 - Only solve for node voltages
 - Once node voltages are known, it is easy to determine any branch variable

Voltage Divider - voltage across R_1

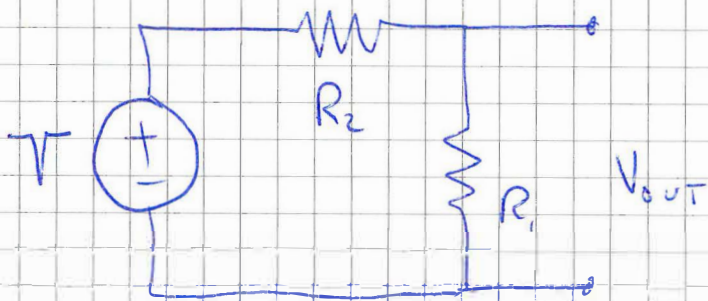

$$V_{out} = \frac{R_1}{R_1 + R_2} V$$


Current Divider - current through R_1

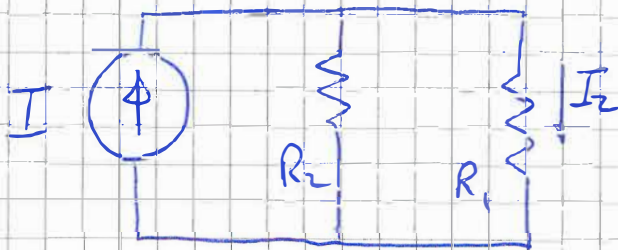

$$I_2 = \frac{R_2}{R_1 + R_2} \cdot I$$

Node Analysis – Basic Procedure

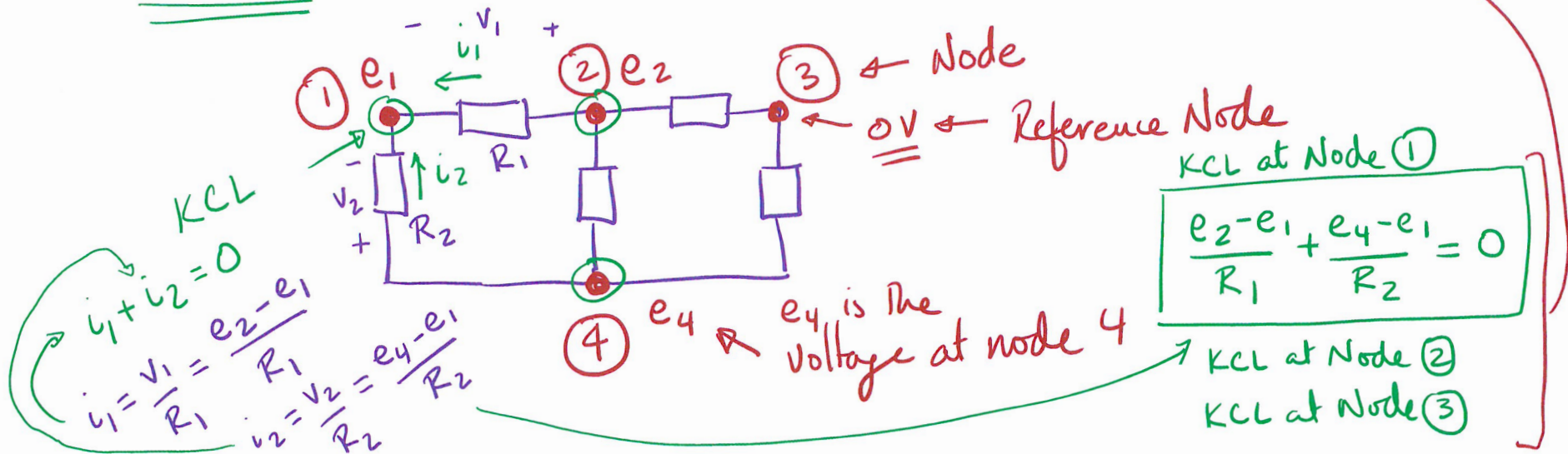- 1) Select a reference node (also called datum node or ground – 0V)
- 2) Specify other node voltages with respect to the reference node ← Implicitly imposes KVL
- 3) Write KCL for nodes with unknown node voltage in terms of node voltages and element constitutive relationships
- 4) Solve for node voltages ← e_1, e_2, e_4
- 5) Back-solve for any required branch voltages and currents




Node Analysis – Comments


- Like the brute force KVL/KCL method, Node Analysis always works
- There is a dual method called Mesh (or more general loop) Analysis in which we set up equations in terms of the independent loop currents
 - If a circuit has fewer independent loops than nodes, the loop analysis method will be faster
 - We will rarely use Mesh Analysis in this course

Selection of Reference Node

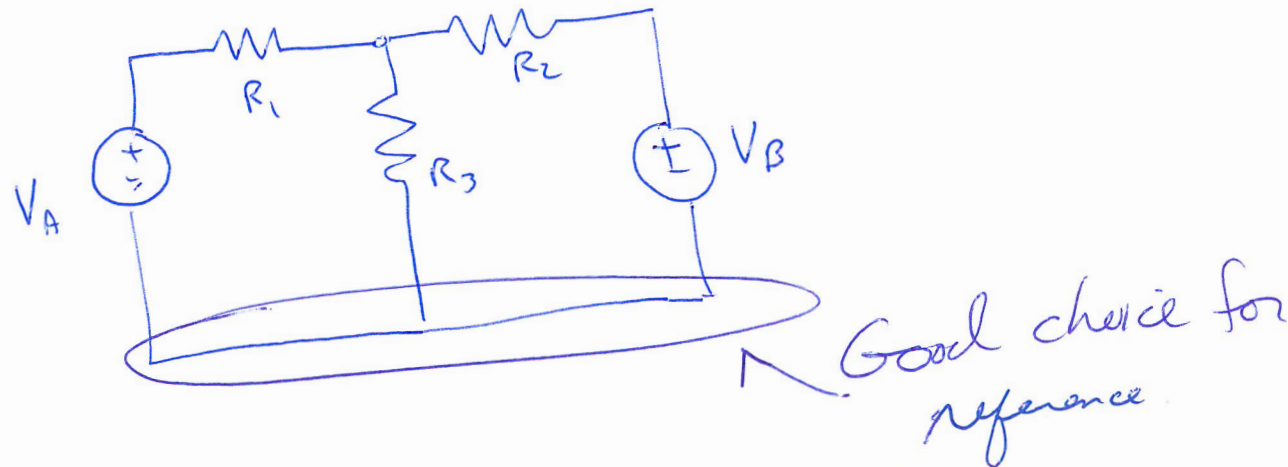- You can pick any node, but some make analysis simpler
 - ① – Good to select node connecting most independent voltage sources (reduces number of unknowns)
 - ② – Good to select node with many elements connected to it (equations are slightly simplified)



Node Analysis Example 1

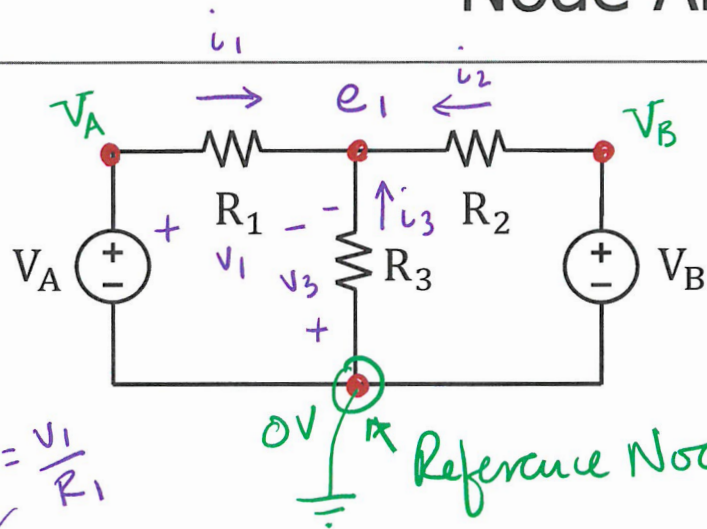

Brute force KVL/KCL method requires 10 equations to be solved

4 nodes

$$i_3 = \frac{v_3}{R_3} = \frac{0 - e_1}{R_3}$$

Conductance
↓
 $G \equiv \frac{1}{R}$

$$i_1 = \frac{v_1}{R_1}$$

KCL @ e_1 : $i_1 + i_2 + i_3 = 0$


$$\Rightarrow \frac{V_A - e_1}{R_1} + \frac{V_B - e_1}{R_2} + \frac{0 - e_1}{R_3} = 0$$

$$\Rightarrow \underline{G_1 V_A} - G_1 e_1 + \underline{G_2 V_B} - G_2 e_1 - G_3 e_1 = 0$$

$$e_1 (G_1 + G_2 + G_3) = G_1 V_A + G_2 V_B \Rightarrow$$

$$e_1 = \frac{G_1 V_A + G_2 V_B}{G_1 + G_2 + G_3}$$

Node Analysis Example 1 (Cont.)

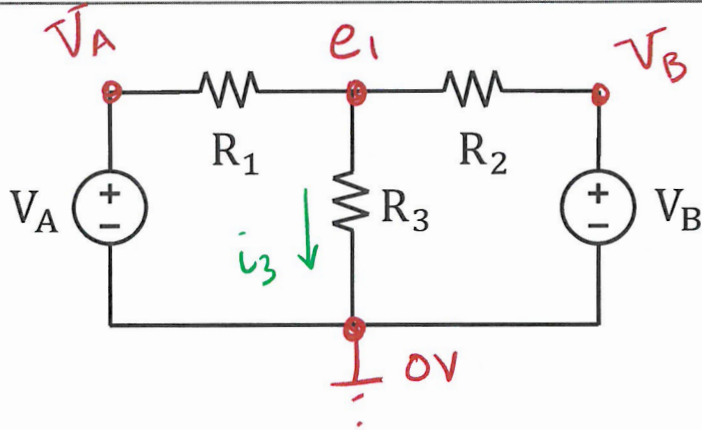


$$e_1 = \frac{G_1 V_A + G_2 V_B}{G_1 + G_2 + G_3}$$

Branch variables (currents and voltages) are now easy to determine

$$i_3 = \frac{e_1 - 0}{R_3} = G_3 \left(\frac{G_1 V_A + G_2 V_B}{G_1 + G_2 + G_3} \right)$$

Node Analysis Example 2

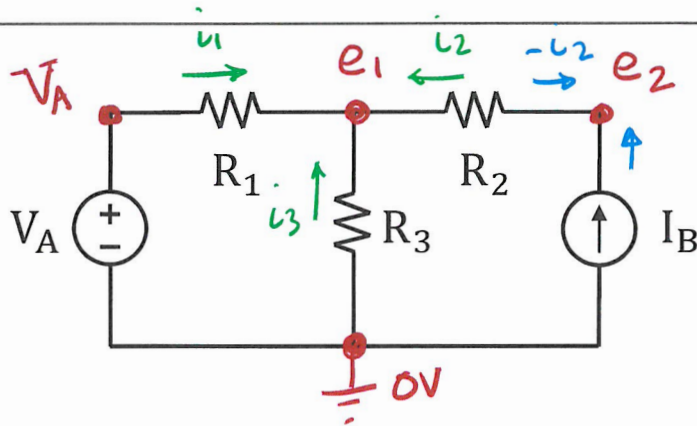

Have replaced one voltage source with a current source

KCL @ e_1

$$i_1 + i_2 + i_3 = 0 \Rightarrow \frac{V_A - e_1}{R_1} + \frac{e_2 - e_1}{R_2} + \frac{0 - e_1}{R_3} = 0 \quad \text{--- (1)}$$

KCL @ e_2

$$-i_2 + I_B = 0 \Rightarrow \frac{e_1 - e_2}{R_2} + I_B = 0 \quad \text{--- (2)}$$

$$\text{(1)} \Rightarrow G_1 V_A - G_1 e_1 + G_2 e_2 - G_2 e_1 - G_3 e_1 = 0 \Rightarrow \boxed{e_1 (G_1 + G_2 + G_3) - G_2 e_2 = G_1 V_A}$$

$$\text{(2)} \Rightarrow \boxed{-G_2 e_1 + G_2 e_2 = -I_B}$$

$$\frac{e_1}{R_2} - \frac{e_2}{R_2} = -I_B$$

$$e_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{e_2}{R_2} = \frac{V_A}{R_1}$$

$$-\frac{e_1}{R_2} + \frac{e_2}{R_2}$$

Node Analysis Example 2 (Cont.)

$$\textcircled{1} \Rightarrow (G_1 + G_2 + G_3)e_1 - G_2e_2 = G_1V_A$$

$$\textcircled{2} \Rightarrow -G_2e_1 + G_2e_2 = I_B$$

Matrix

$$\begin{bmatrix} (G_1 + G_2 + G_3) & -G_2 \\ -G_2 & G_2 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1V_A \\ I_B \end{bmatrix}$$

Solving 2x2 Matrix Equations

$$\left. \begin{array}{l} a_{11}x_1 + a_{12}x_2 = b_1 \\ a_{21}x_1 + a_{22}x_2 = b_2 \end{array} \right\} \Rightarrow \begin{array}{c} \text{known} \\ \left[\begin{array}{cc} a_{11} & a_{12} \\ a_{21} & a_{22} \end{array} \right] \begin{array}{c} \text{unknowns} \\ \left[\begin{array}{c} x_1 \\ x_2 \end{array} \right] = \left[\begin{array}{c} b_1 \\ b_2 \end{array} \right] \\ \text{known} \end{array} \end{array} \Rightarrow \underline{\underline{A\bar{x} = \bar{b}}}$$

$$A\bar{x} = \bar{b} \Rightarrow \underline{\underline{\bar{x} = A^{-1}\bar{b}}} \quad \text{where } \boxed{A^{-1} = \frac{\text{adj}(A)}{\det(A)}}$$


$$\begin{array}{c} \text{diagonal} \\ \left[\begin{array}{cc} a_{11} & a_{12} \\ a_{21} & a_{22} \end{array} \right] \begin{array}{c} x_1 \\ x_2 \end{array} = \begin{array}{c} b_1 \\ b_2 \end{array} \end{array} \Rightarrow \begin{array}{c} \left[\begin{array}{c} x_1 \\ x_2 \end{array} \right] = \frac{1}{\det(A)} \left[\begin{array}{cc} a_{22} & -a_{12} \\ -a_{21} & a_{11} \end{array} \right] \begin{array}{c} b_1 \\ b_2 \end{array} \\ \text{adj}(A) \end{array}$$


$$\text{where } \underline{\underline{\det(A) = a_{11}a_{22} - a_{12}a_{21}}}$$

$$x_1 = \frac{a_{22}b_1 - a_{12}b_2}{\det(A)}$$

$$x_2 = \frac{-a_{21}b_1 + a_{11}b_2}{\det(A)}$$

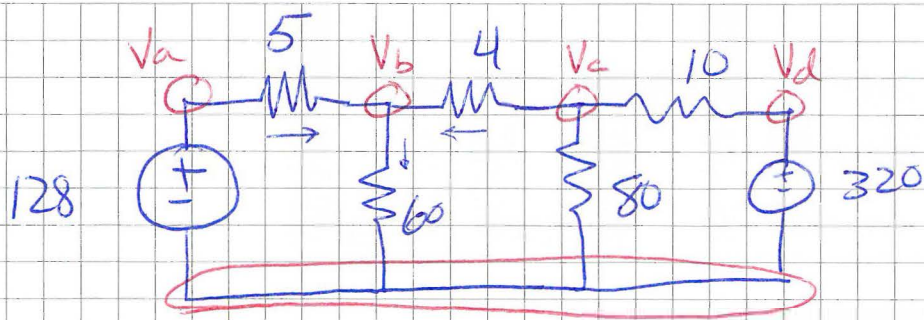Adjoint of 2x2
 swap a_{11} and a_{22}
 change sign of a_{12}, a_{21}





4 nodes plus reference

We can see $V_a = 128V$
 $V_d = 320$

So we need to write the node equations for V_b and V_c

Node b
$$\frac{128 - V_b}{5} - \frac{V_b}{60} + \frac{V_c - V_b}{4} = 0$$

Node c
$$\frac{V_b - V_c}{4} - \frac{V_c}{80} + \frac{320 - V_c}{10} = 0$$

Consolidate (b)
$$-V_b \left(\frac{1}{5} + \frac{1}{60} + \frac{1}{4} \right) + V_c \left(\frac{1}{4} \right) = -\frac{128}{5}$$

(c)
$$V_b \left(\frac{1}{4} \right) - V_c \left(\frac{1}{4} + \frac{1}{80} + \frac{1}{10} \right) = -\frac{320}{10}$$

There are clearly some common factors here that can be used to simplify the calculation. Nevertheless I'll just use my calculator to compute values

(b) $-0.4667 V_b + 0.25 V_c = -25.6$

(c) $0.25 V_b - 0.362 V_c = -32$

2 eq, 2 unknowns

We can solve this easily by hand, but for larger systems one usually uses linear algebra

$$\begin{bmatrix} -0.4167 & 0.25 \\ 0.25 & -0.3621 \end{bmatrix} \begin{bmatrix} V_b \\ V_c \end{bmatrix} = \begin{bmatrix} -25.6 \\ -32 \end{bmatrix}$$

$$V_b = 162.24 \quad V_c = 200.44$$

(If I cleared fractions, I get 162 and 200)


Does this make sense?

Test V_b , determine current in each resistor.

$$5\Omega \quad \frac{128 - 162}{5} = -6.8 \text{ A} \quad \left. \vphantom{\frac{128 - 162}{5}} \right\} = -9.5$$

$$60\Omega \quad -\frac{162}{60} = -2.7 \text{ A}$$

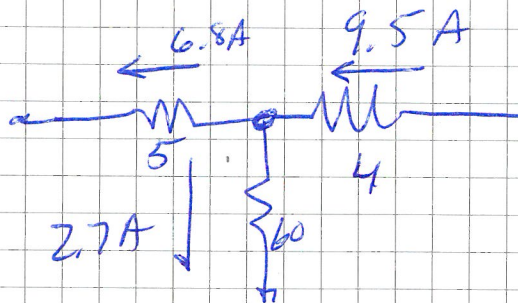
$$4\Omega \quad \frac{200 - 162}{4} = +9.5 \text{ A}$$



$$\Sigma i = 0$$

Mesh Analysis

What if we had a circuit like this?

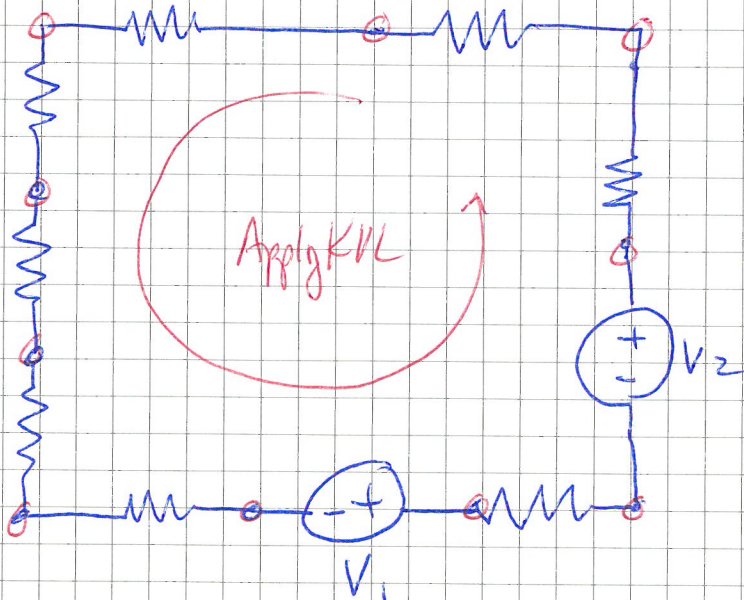


10 nodes
 9 independent equations
 (not to mention
 2 supernodes)

In cases like this node analysis is more cumbersome than other methods, notably loop or mesh

KVL will yield one equation, giving us i . From that we can find all voltages

We could apply it to the earlier example

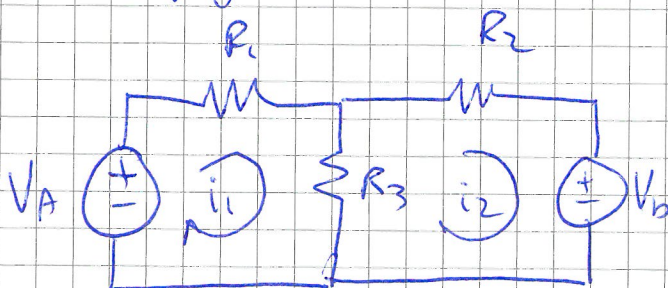

$$-V_A + i_1 R_1 + (i_1 - i_2) R_3 = 0$$

$$+V_b + (i_2 - i_1) R_3 + i_2 R_2 = 0$$

2 eq, 2 unknowns