

ECE/ENGRD 2100

Introduction to Circuits for ECE



Lecture 40

DC-DC Power Converters

Announcements

- Upcoming due dates:
 - Lab report 6 due by 11:59 pm on Friday May 3, 2019
 - Homework 6 due by 11:59 pm on Thursday May 9, 2019


AC-AC Voltage Conversion

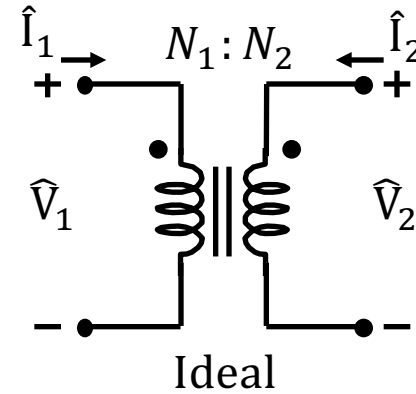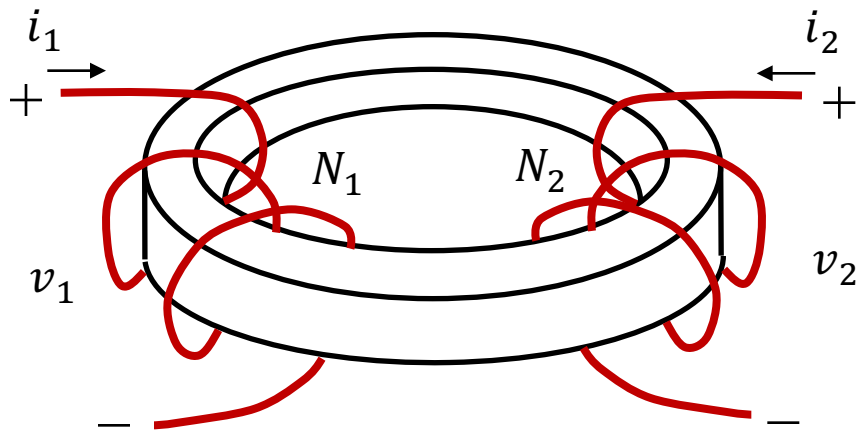

$$\frac{\hat{V}_2}{\hat{V}_1} = \frac{N_2}{N_1}$$

$$\frac{\hat{I}_2}{\hat{I}_1} = -\frac{N_1}{N_2}$$

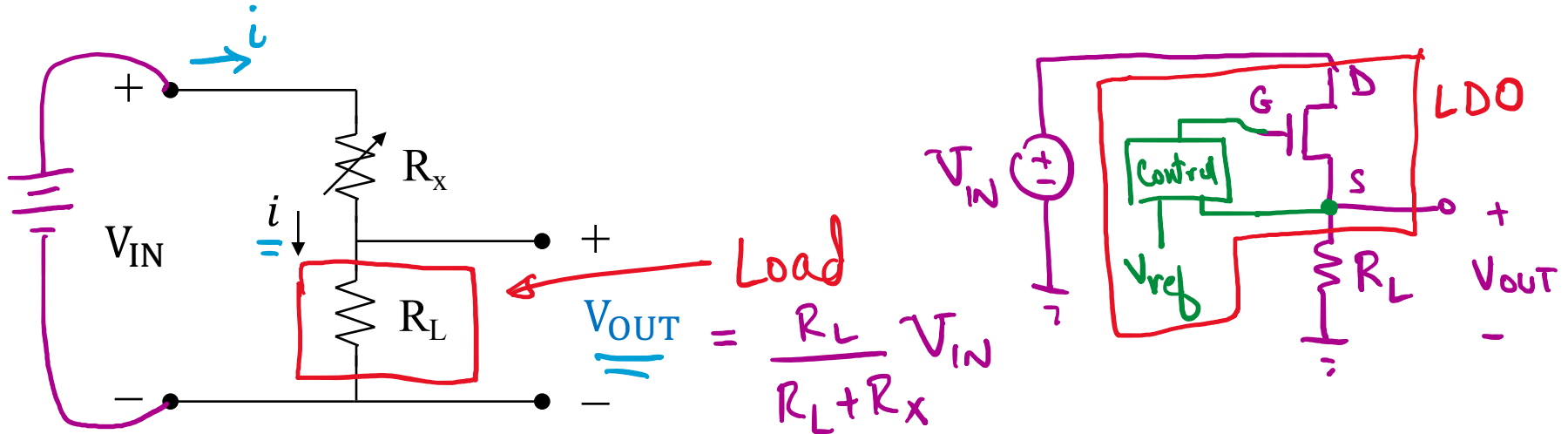DC-DC Voltage Conversion - Linear Regulator




Efficiency, $\eta \equiv \frac{\text{Output Power}}{\text{Input Power}} = \frac{V_{OUT} i}{V_{IN} i}$


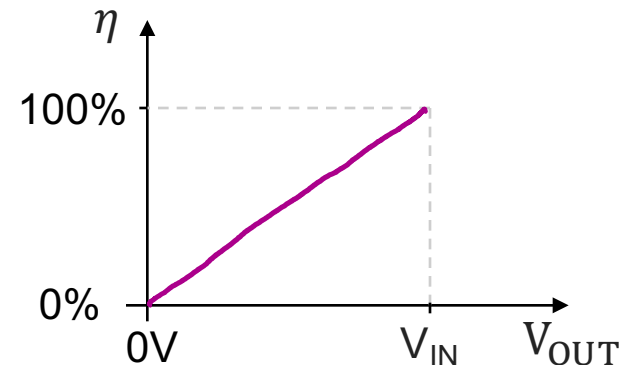
Example: $V_{IN} = 12\text{ V}$

$V_{OUT} = 5\text{ V} \Rightarrow \eta = \frac{5}{12} \approx 42\%$



$V_{OUT} = 1\text{ V} \Rightarrow \eta = \frac{1}{12} \approx 8\%$



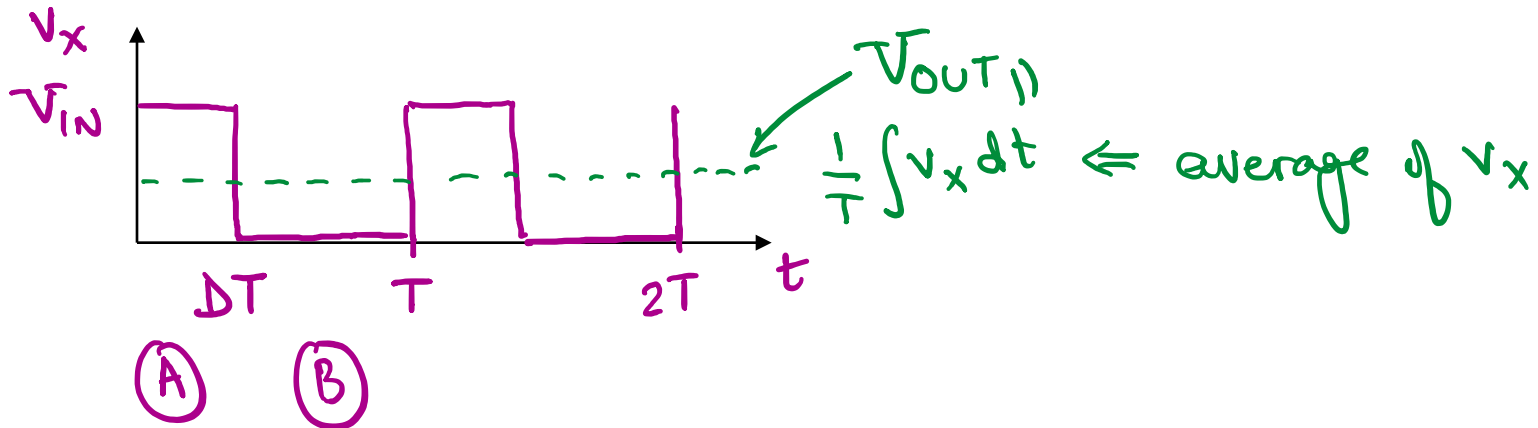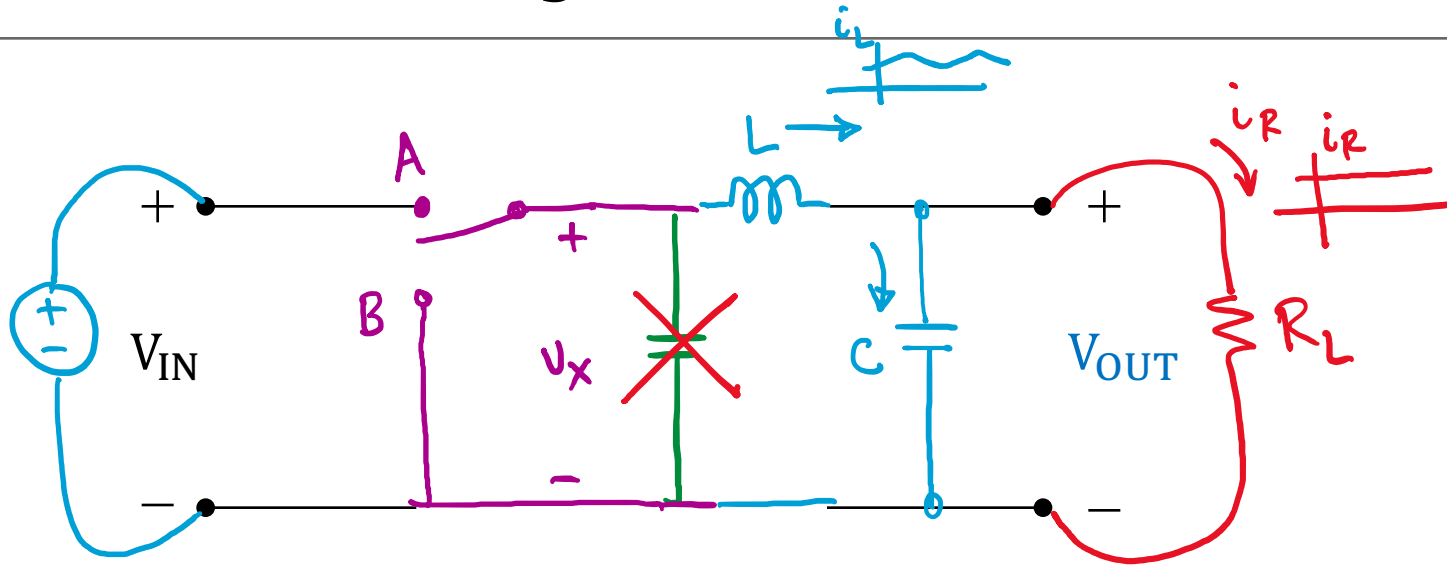DC-DC Voltage Conversion – Alternate Approach




Switching Power Converter

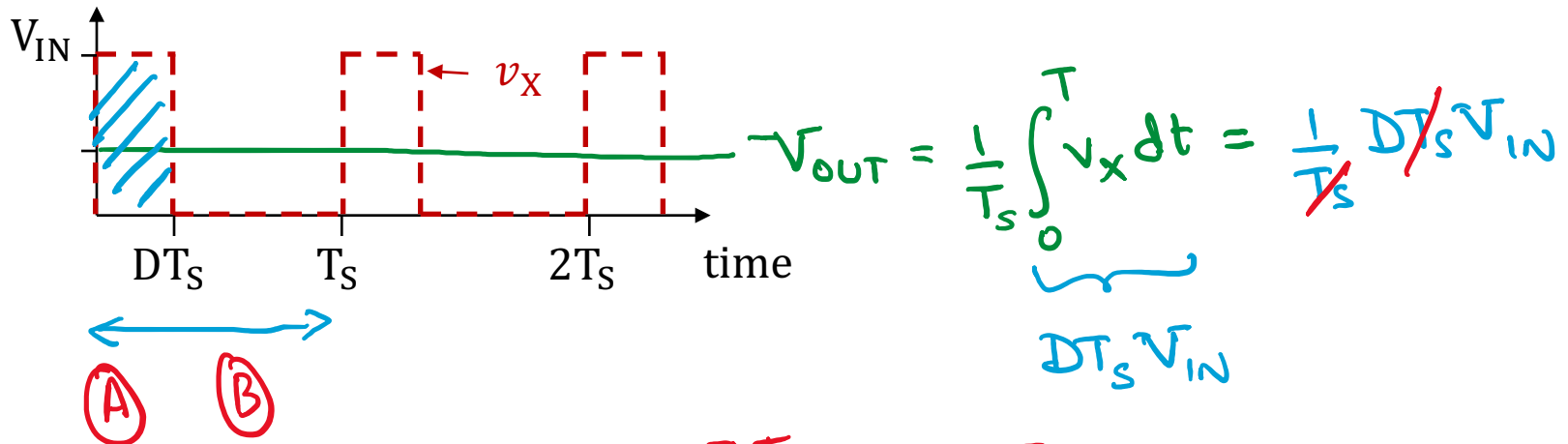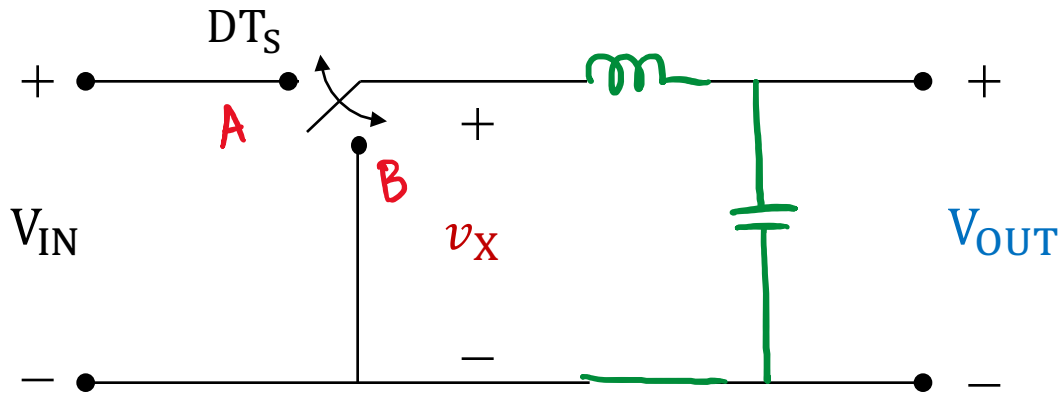

$$V_{OUT} = D V_{IN}$$

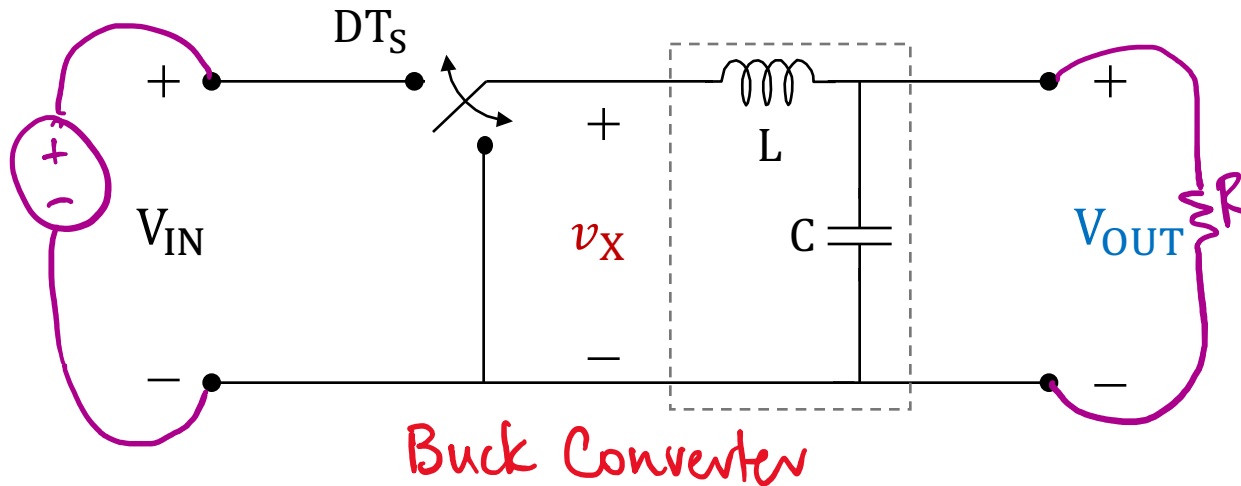Switching Power Converter with Low Pass Filter




D = switch duty cycle
 $0 \leq D \leq 1$

T_S = switching period


f_S = switching frequency
 $= 1/T_S$

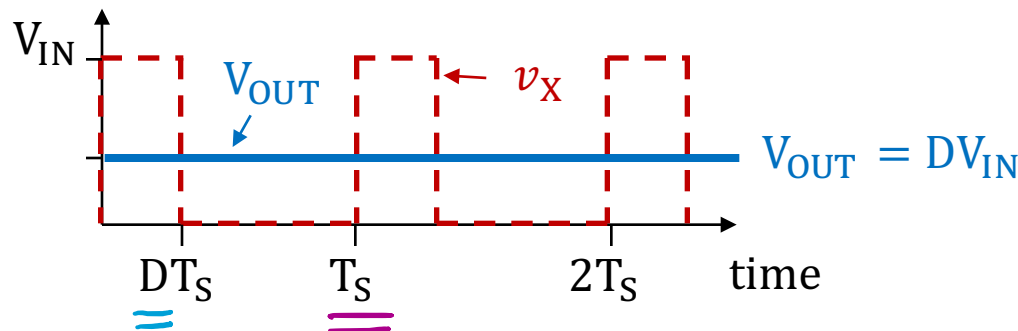f_0 = filter cutoff frequency
 $= 1/2\pi\sqrt{LC}$



- Choose filter cutoff frequency f_0 much smaller than switching frequency f_S
- This circuit is known as the “buck converter”

Power Loss in an Ideal Switch

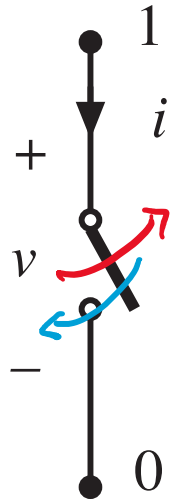


Switch closed: $v(t) = 0$

Switch open: $i(t) = 0$

$$\text{Power loss: } p(t) = v(t) i(t) = \overset{\text{closed}}{0} (I) + \overset{\text{open}}{V} (0) = 0 + 0 = 0$$


Efficiency of Switching Power Converter

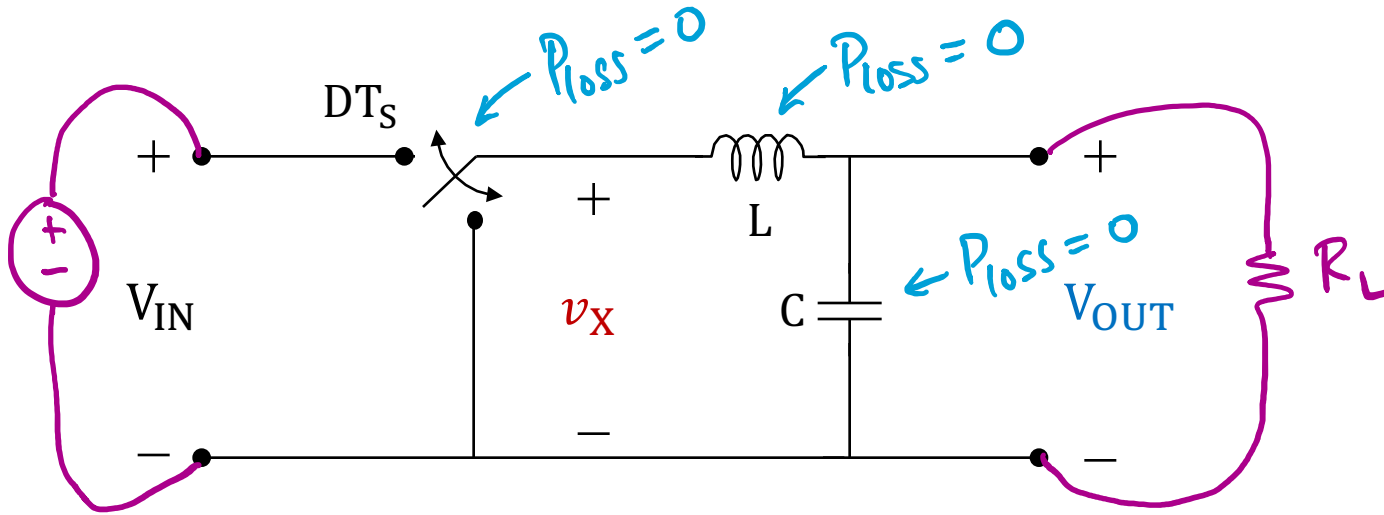



$$\eta = \frac{P_{OUT}}{P_{IN}} = \frac{P_{OUT}}{P_{OUT} + \underbrace{P_{LOSS}}_{=0}} = \frac{P_{OUT}}{P_{OUT}} = 100\%$$

$$P_{OUT} = P_{IN}$$


$$V_{OUT} I_{OUT} = V_{IN} I_{IN}$$

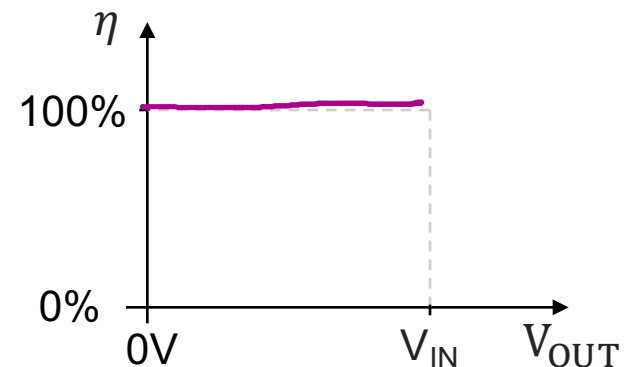

Switch Implementation of Buck Converter

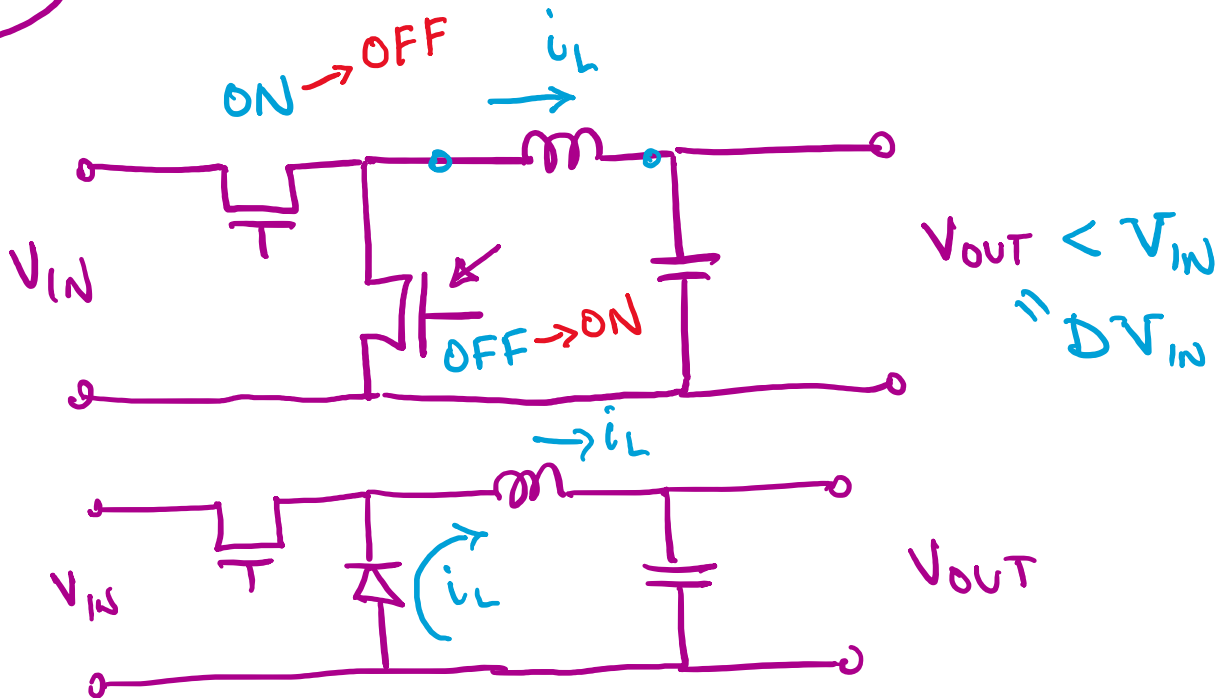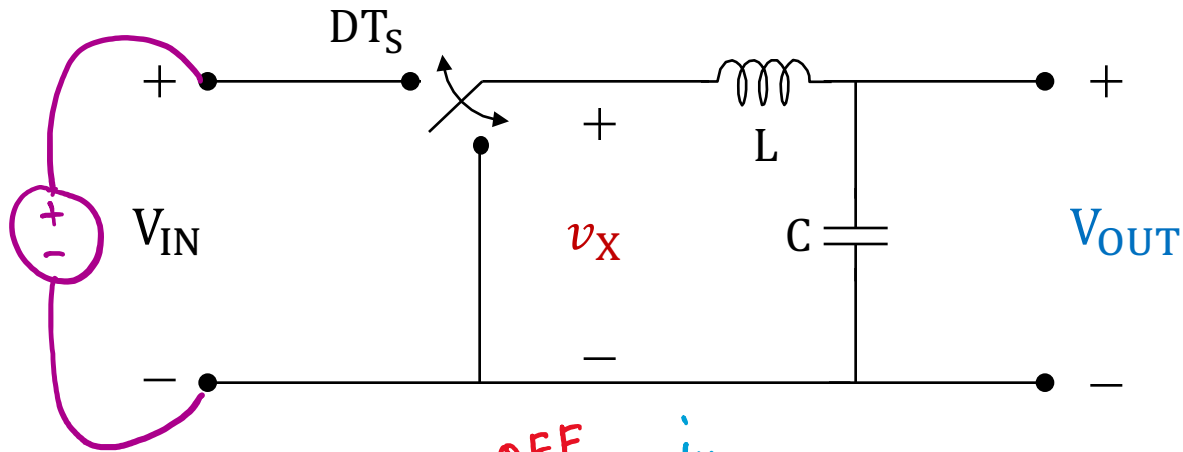


Boost Converter

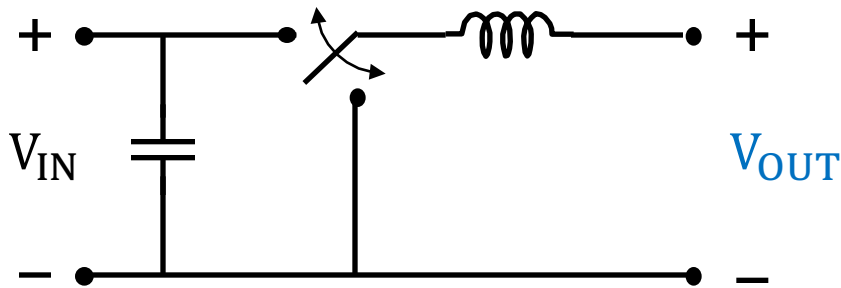


Buck Converter

$$V_L = L \frac{di_L}{dt}$$

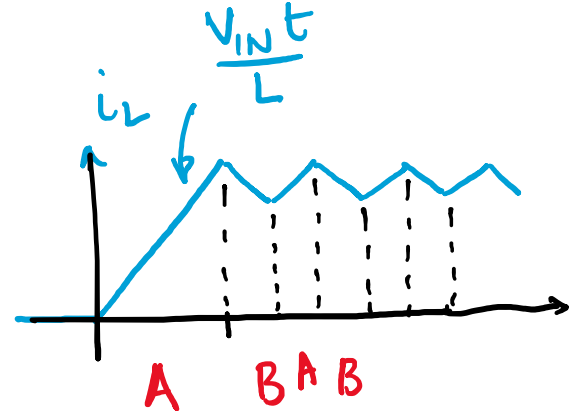


- Swap source and load


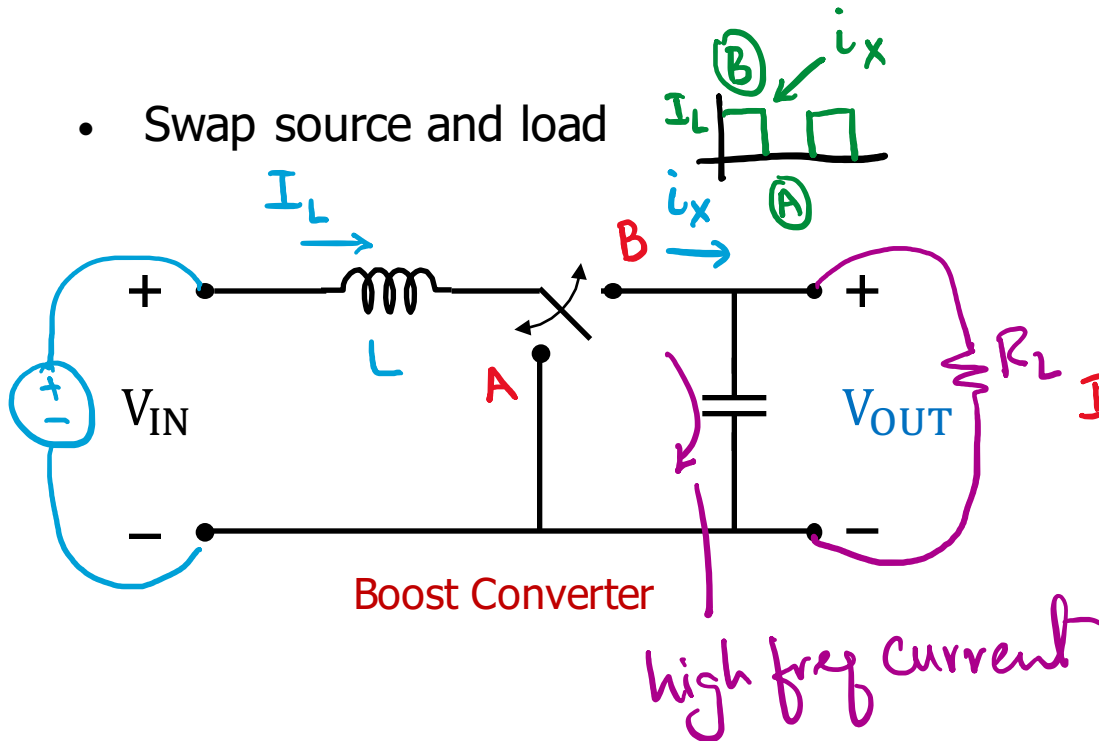


Boost Converter

high freq current

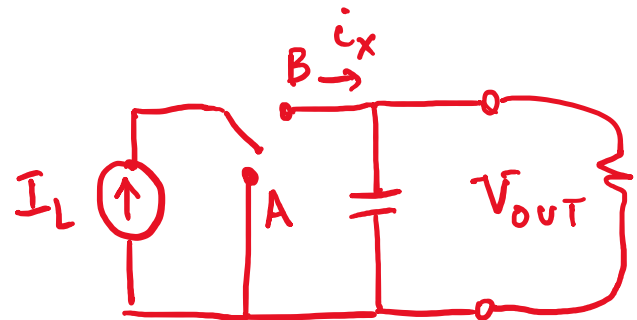


Switch Implementation of Boost Converter

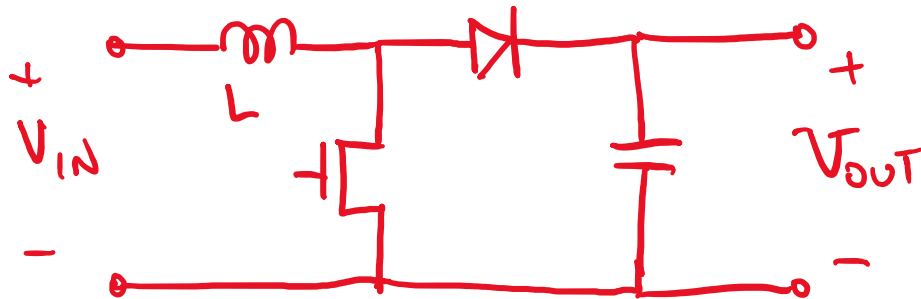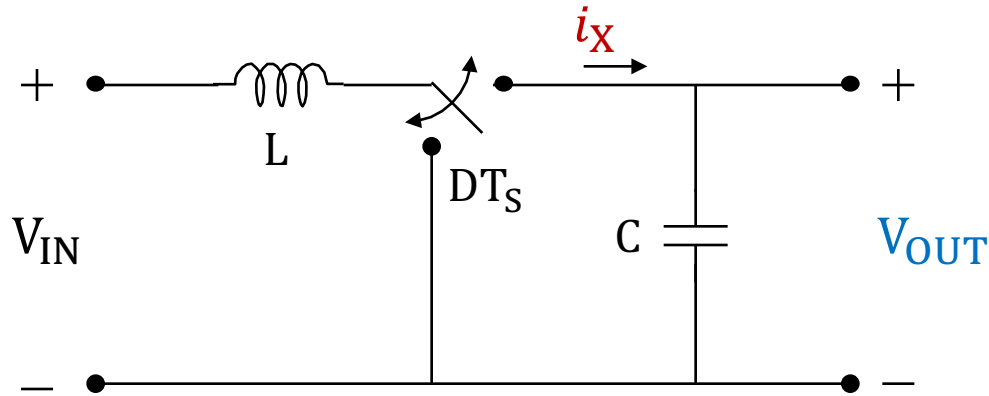

Sample Power Converters

DC-DC Power Converter

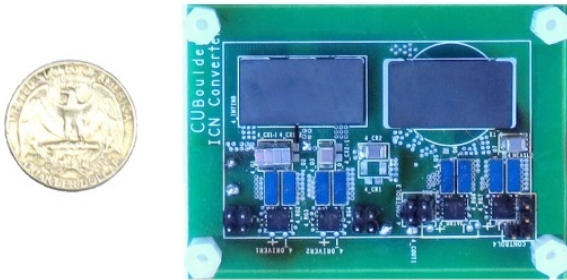


550-W quarter-brick telecom intermediate bus dc-dc converter

AC-DC Converter (Rectifier)




Laptop charger

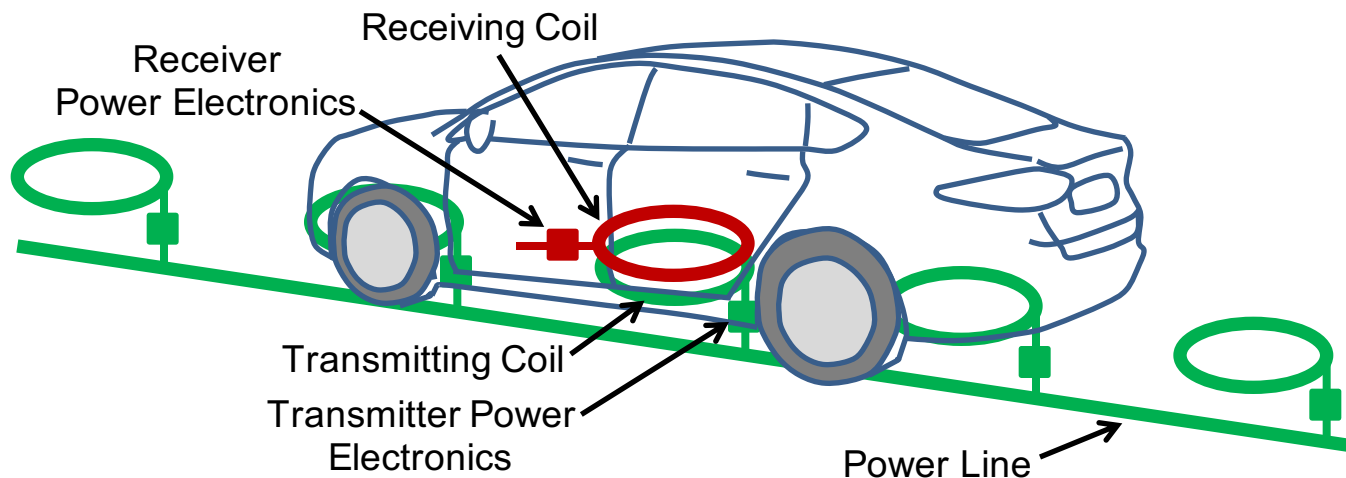Dynamic Wireless Charging of Electric Vehicles




Dynamic Capacitive Wireless Charging

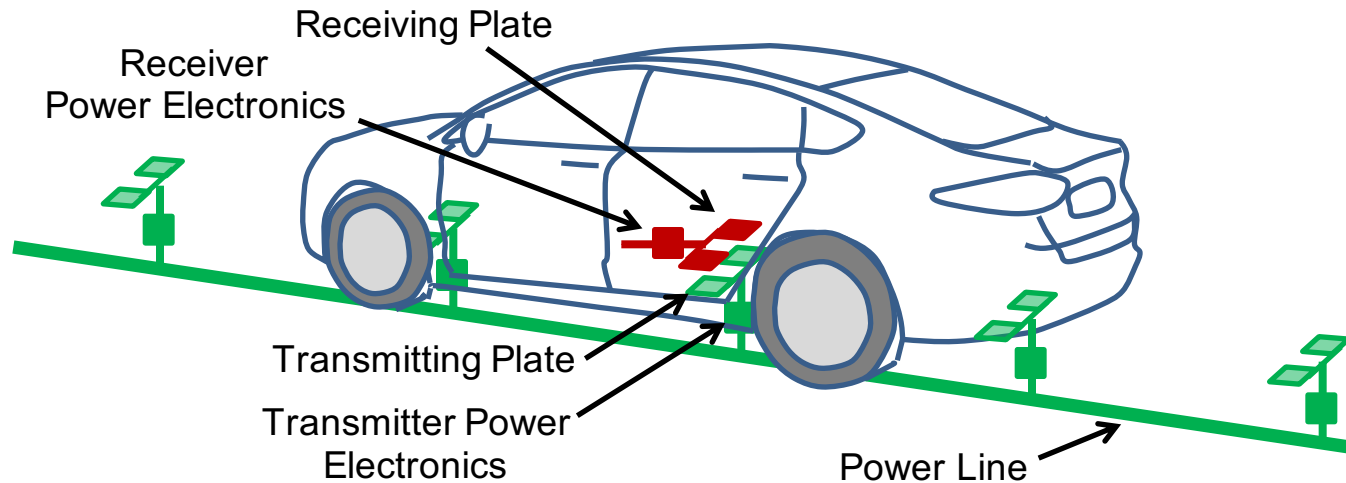


- Capacitive WPT systems do not have ferrites and can be:
 - Less expensive
 - More efficient
 - Smaller
 - Lighter
 - Easier to embed in roadway


Capacitive Wireless Charging Prototypes

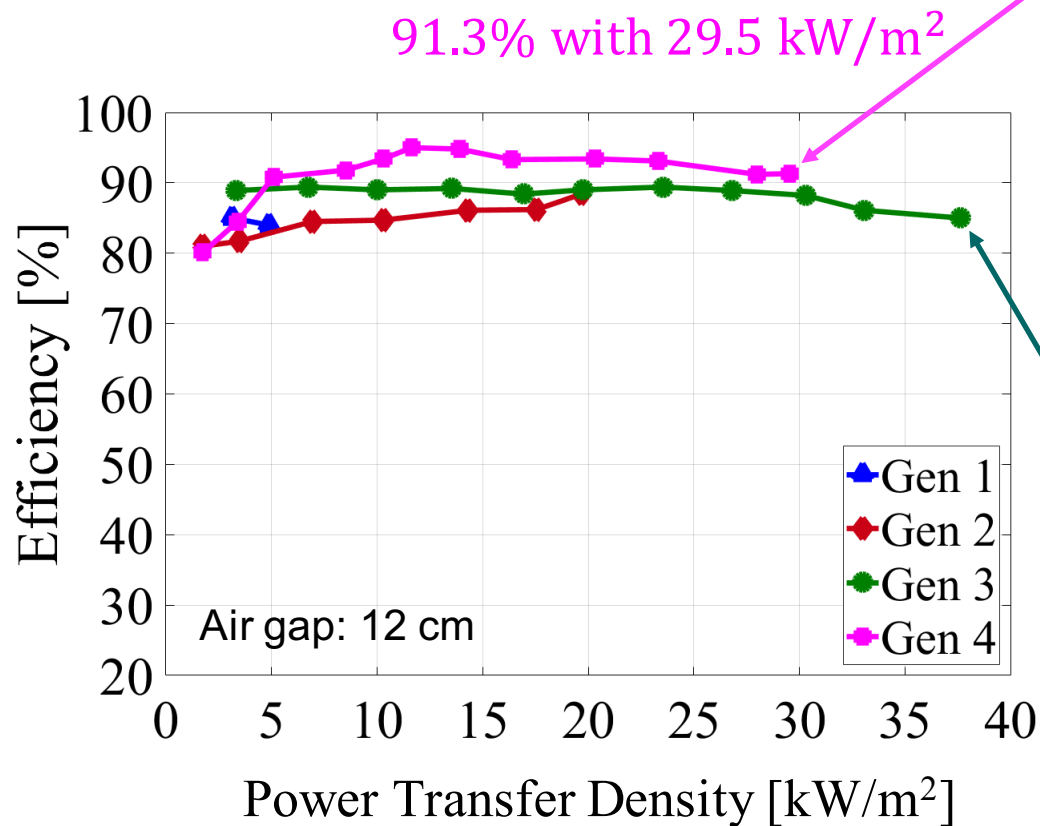

Gen 4 System:
13.56-MHz 0.9-kW

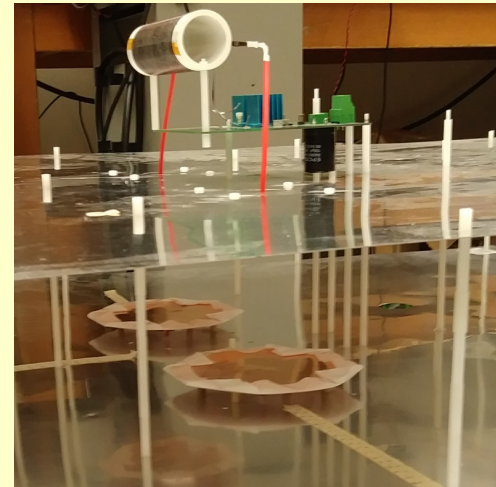

Gen 3 System: 6.78-MHz 1.2-kW

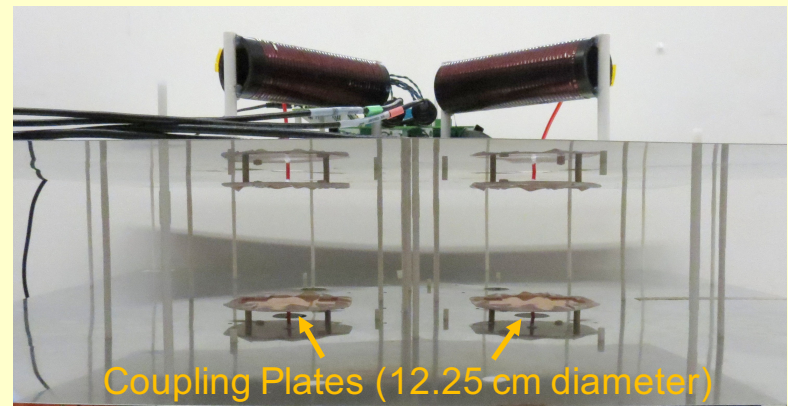

Power Electronics – ECE 4950

Title:	Power Electronics
Course Number:	ECE 4950
Credits:	4
Next Offering:	Fall 2019
Lecture:	MWF 10:10-11:00 am
Discussion:	W 1:25-2:15 pm
Prerequisite:	ECE 3150 (Microelectronics) or equivalent
Instructor:	Khurram Afridi