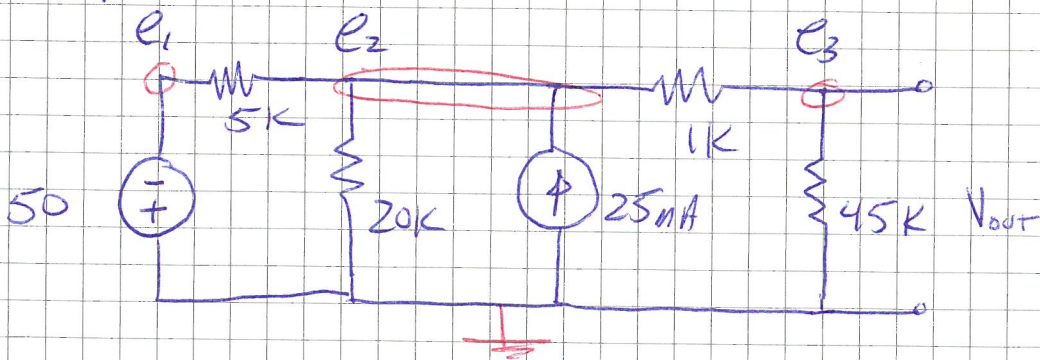


Node Analysis

- ① Make a neat drawing of circuit
- ② Mark and label every node
- ③ Select one node to be the reference (because voltages are always defined with respect to something)
- ④ Write KCL for each node (except the reference)
- ⑤ Solve for the node voltages
- ⑥ As needed, determine the currents.

Example 1



What is V_{out} ?

3 nodes + reference.

$$e_1 = -50V$$

So we only need 2 eqs.

$$\frac{-50 - e_2}{5k} + \frac{0 - e_2}{20k} + 25mA + \frac{e_3 - e_2}{1k} = 0$$

$$\frac{e_2 - e_3}{1k} + \frac{0 - e_3}{45k} = 0$$

Consolidate

$$-e_2 \left(\frac{1}{5K} + \frac{1}{20K} + \frac{1}{1K} \right) + e_3 \left(\frac{1}{1K} \right) = \frac{50}{5K} - 25_{mA} = -15_{mA}$$

$$e_2 \left(\frac{1}{1K} \right) - e_3 \left(\frac{1}{1K} + \frac{1}{45K} \right) = 0$$

Clear the denominators


$$-e_2 (4 + 1 + 20) + e_3 \cdot 20 = -300$$

$$e_2 \cdot 45 - e_3 \cdot 46 = 0$$


(Voltage divider!)

Solve 2 eqs

$$e_2 = 55.2 \quad e_3 = 54$$

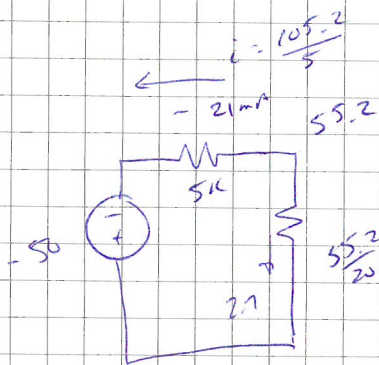

Example 2

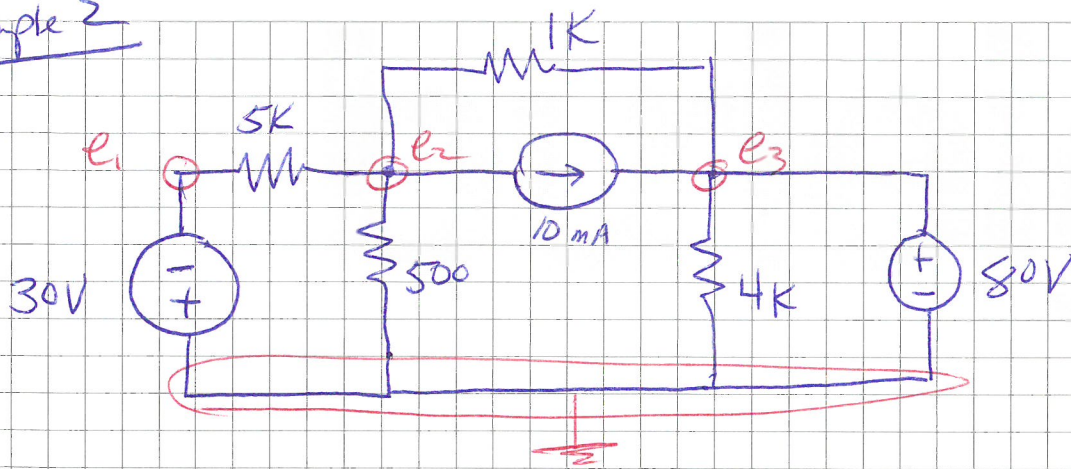

$$e_1 = -30$$

$$e_3 = 80$$

$$e_2 \quad \frac{-30 - e_2}{5k} + \frac{0 - e_2}{500} + \frac{80 - e_2}{1000} - 10mA = 0$$

Consolidate

$$\begin{aligned} -e_2 \left[\frac{1}{5000} + \frac{1}{500} + \frac{1}{1000} \right] &= 10mA + \frac{30}{5000} - \frac{80}{1000} \\ &= 10mA + 6mA - 80mA \\ &= 64mA \end{aligned}$$

Clear fractions by multiplying by 5000


$$-e_2 [1 + 10 + 5] = 5.64$$

$$e_2 = \frac{-5.64}{16} = \underline{\underline{-20V}}$$

Notice the 4k resistor had no impact - it was parallel to a voltage source.


Standard Node Analysis Limitations

- There are a few situations where standard Nodal Analysis does not work
 - One of these situations is when the circuit has a floating independent voltage source (i.e., voltage source is not connected to the ground node either directly or via another independent voltage source)
 - Standard node analysis does not work since the current of an independent voltage source is not a function of the voltage across it – hence it is not possible to write KCL in terms of node voltages and constitutive relationships

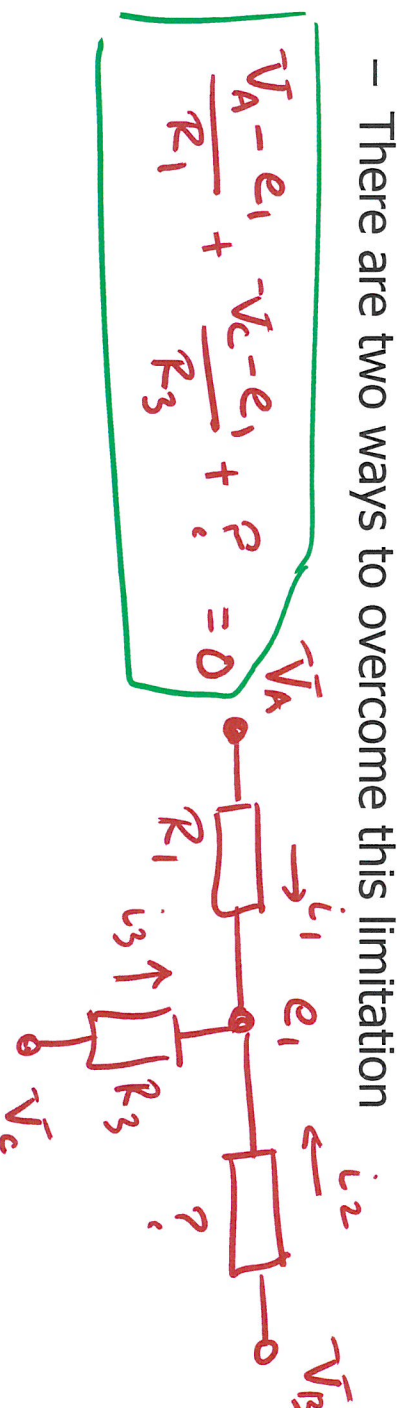


Node Analysis Example 3

Only unknown

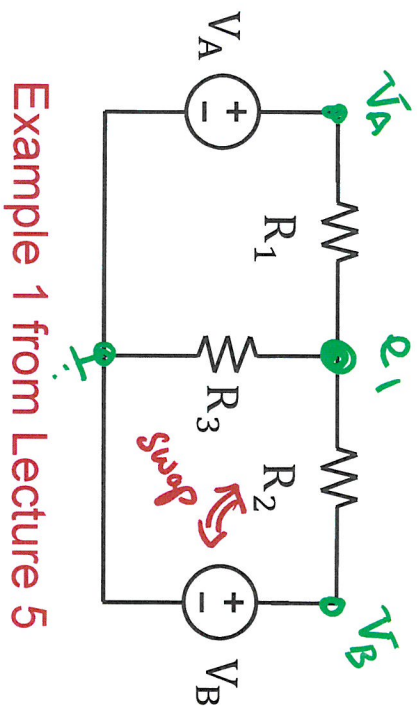

Example 1 from Lecture 5


Do this circuit

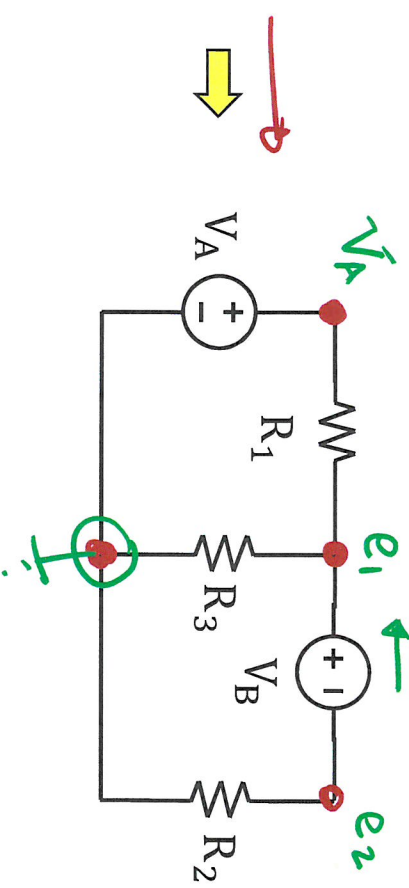

Don't know how to write i_B in terms of e_1 and e_2

Therefore, can't apply Basic Node Analysis
 will have to Modify Node Analysis

Node Analysis Example 3 – Method 1

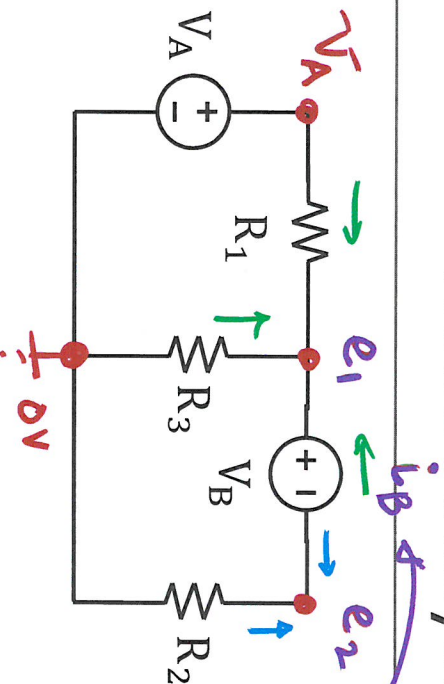

Modified Node Analysis
(used by computer programs
such as SPICE)

Create new unknown

$$\underline{i_B}$$

KCL @ e₁

$$\frac{V_A - e_1}{R_1} + \frac{0 - e_1}{R_3} + i_B = 0 \quad \text{--- (1)}$$

Have 3 unknowns
 e_1, e_2, i_B


KCL @ e₂

$$\frac{0 - e_2}{R_2} - i_B = 0 \quad \text{--- (2)}$$

3rd Eqn comes from constitutive relationship of V_B

$$e_1 - e_2 = V_B \quad \text{--- (3)}$$

Node Analysis Example 3 – Method 2

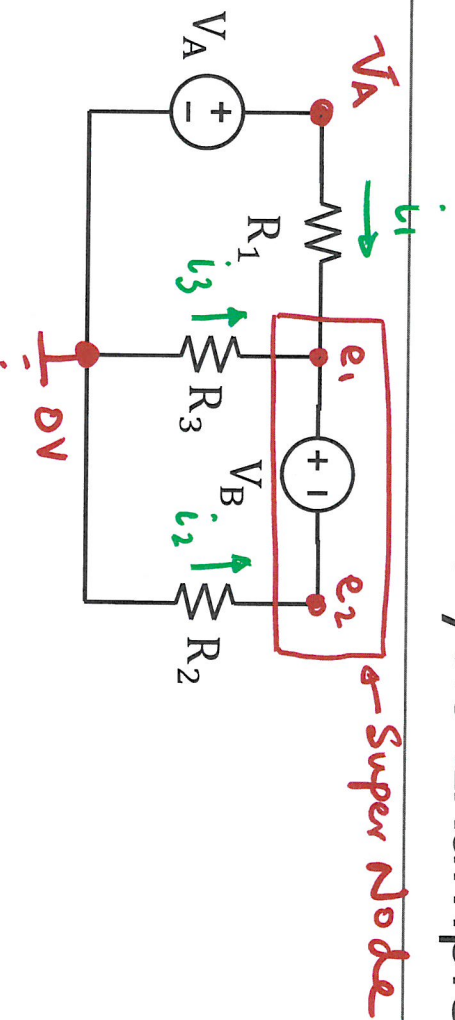

Super Node Method

Apply KCL to the Super Node

$$i_1 + i_2 + i_3 = 0 \Rightarrow$$


$$\frac{V_A - e_1}{R_1} + \frac{0 - e_2}{R_2} + \frac{0 - e_1}{R_3} = 0 \quad \text{--- (1)}$$

2nd Eqn :

$$e_1 - e_2 = V_B \quad \text{--- (2)}$$

Combine
Relationship of V_B

Solve for e_1 & e_2

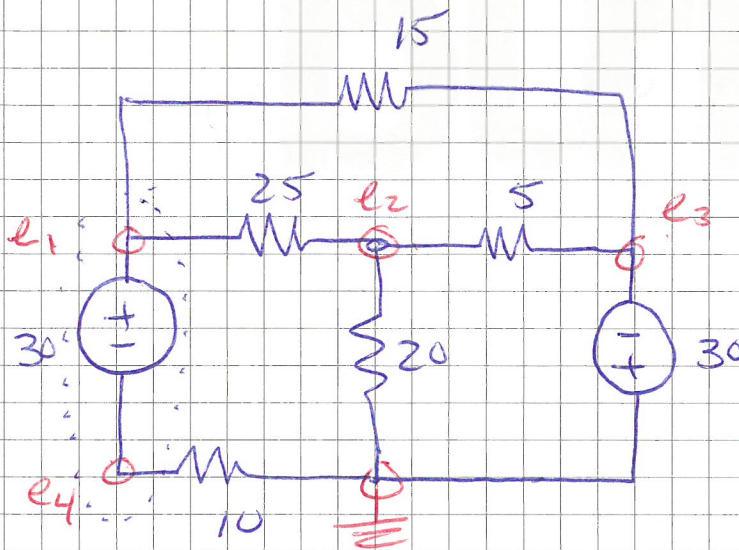

① Pick nodes 5 nodes set one to Ground

② Note $e_3 = -30V$

③ Define super node $e_1 - e_4$

④ Write KCL

$$e_1 - e_4 \quad \frac{0 - e_4}{10} + \frac{e_2 - e_1}{25} + \frac{-30 - e_1}{15} = 0$$

$$e_2 \quad \frac{e_1 - e_2}{25} + \frac{0 - e_2}{20} + \frac{-30 - e_2}{5} = 0$$

$$e_3 = -30$$

} 3 eq.

Finally $e_1 = e_4 + 30$