

ECE/ENGRD 2100

Introduction to Circuits for ECE





Lecture 9

Large-Signal Analysis of Nonlinear Circuits



Announcements

- Upcoming due dates:
 - Prelab 2 due by 12:20 pm on Tuesday February 12, 2019
 - Homework 2 due by 11:59 pm on Friday February 15, 2019
 - Lab report 2 due by 11:59 pm on Friday February 22, 2019
- Lab 2 is this week (starting Tuesday February 12, 2019)
- Prelim 1 on Thursday February 21, 2019 from 7:30 – 9 pm in 203 Phillips

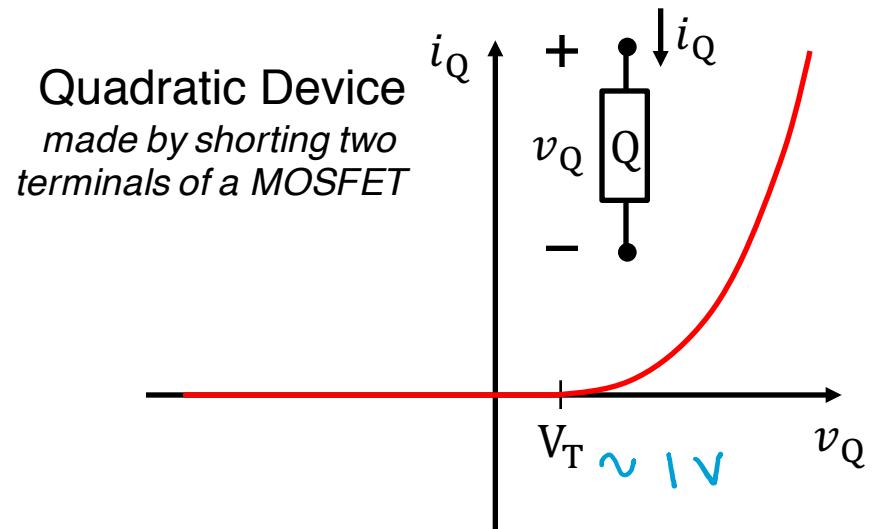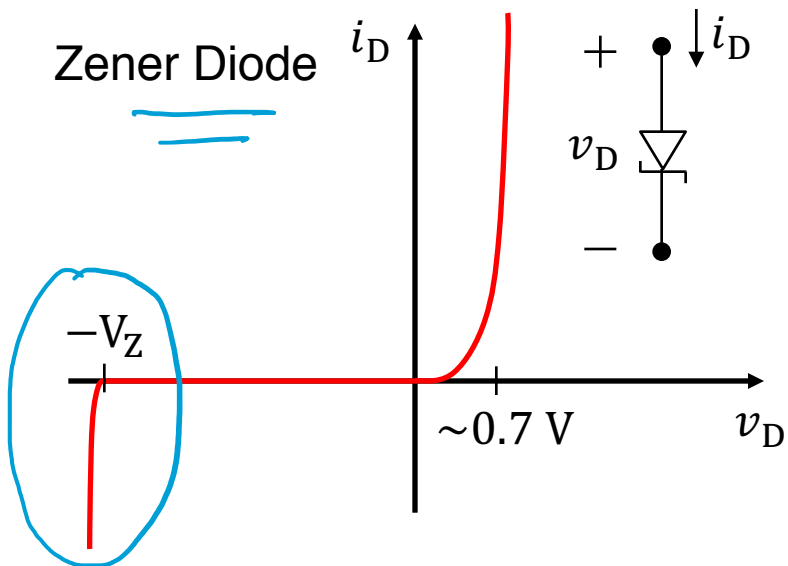
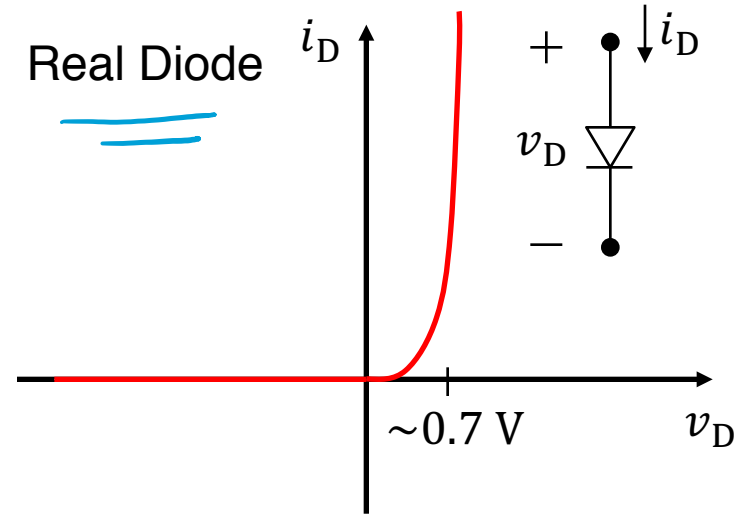
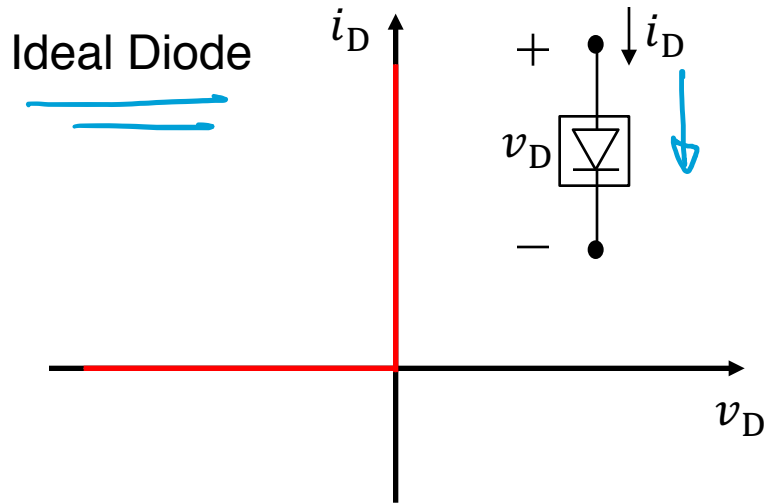
Examples of Two-Terminal Nonlinear Devices




Analysis of Circuits with Nonlinear Devices

- Following techniques **still work** when circuits have nonlinear components:
 - Brute Force (KVL, KCL and Element Constitutive Relationships)
 - Mesh and Loop Analysis
 - Node Analysis 
 - Superposition **does not** work when circuits have nonlinear components
- Handwritten blue notes:*  non-linear fn
non-linear device

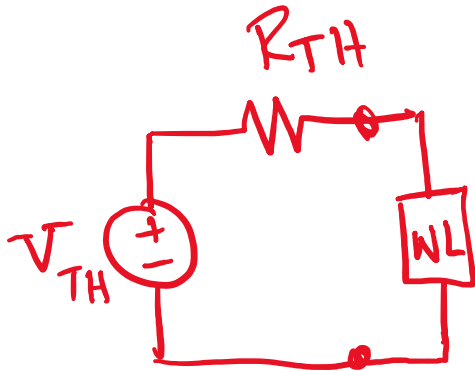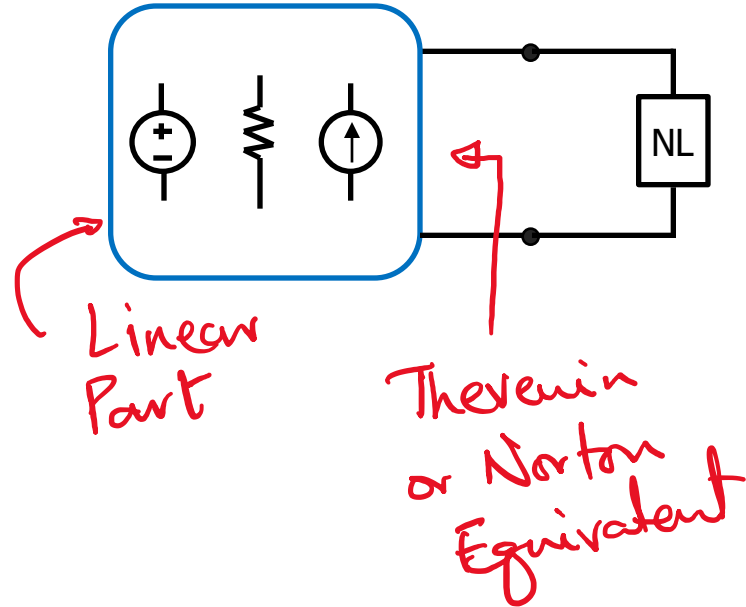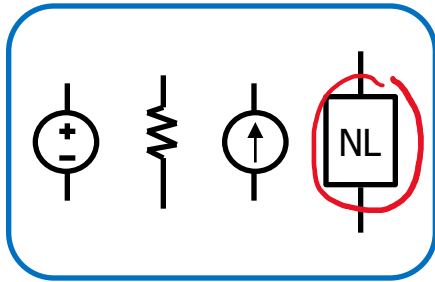
Analysis of Circuits with One Nonlinear Device



Nonlinear Device Circuit – Example 1

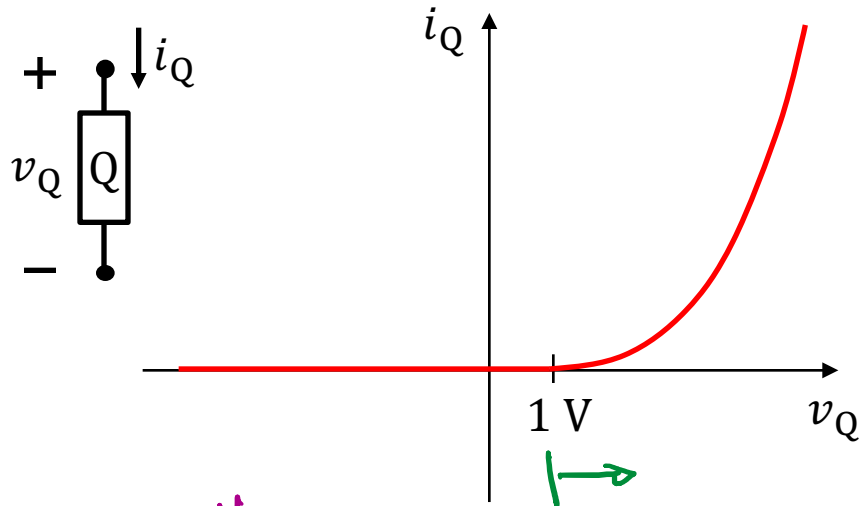
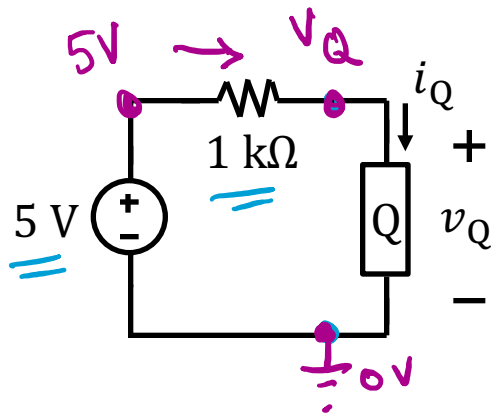
$$i_Q = \begin{cases} 0 & \text{if } v_Q < 1\text{ V} \\ 0.5(v_Q - 1)^2 \text{ mA} & \text{if } v_Q \geq 1\text{ V} \end{cases}$$




$$\frac{5 - v_Q}{1\text{ k}\Omega} = i_Q$$

Try Assuming $v_Q < 1\text{ V} \Rightarrow i_Q = 0$

$$\frac{5 - v_Q}{1\text{ k}\Omega} = 0 \Rightarrow \underline{v_Q = 5\text{ V}} \quad \times$$

Not consistent with assumption

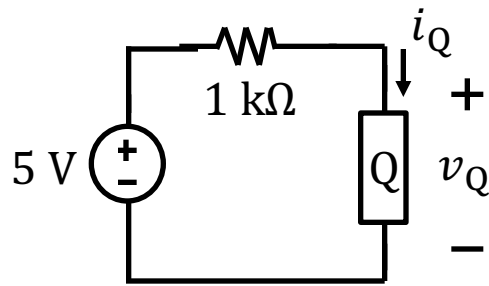Nonlinear Device Circuit – Example 1 (Cont.)



$$i_Q = \begin{cases} 0 & \text{if } v_Q < 1 \text{ V} \\ 0.5(v_Q - 1)^2 \text{ mA} & \text{if } v_Q \geq 1 \text{ V} \end{cases}$$

Try $v_Q \geq 1 \text{ V} \Rightarrow i_Q = 0.5(v_Q - 1)^2 \text{ mA}$

$$\frac{5 - v_Q}{1 \text{ k}\Omega} = i_Q = 0.5(v_Q - 1)^2 \text{ mA} \Rightarrow 5 - v_Q = 0.5(v_Q - 1)^2$$


$$10 - 2v_Q = v_Q^2 - 2v_Q + 1 \Rightarrow v_Q^2 = 9 \Rightarrow \underline{v_Q = \pm 3}$$

-ve value is non-physical

$$\Rightarrow v_Q = +3 \text{ V}$$

$$i_Q = 0.5(3 - 1)^2 = \underline{2 \text{ mA}}$$

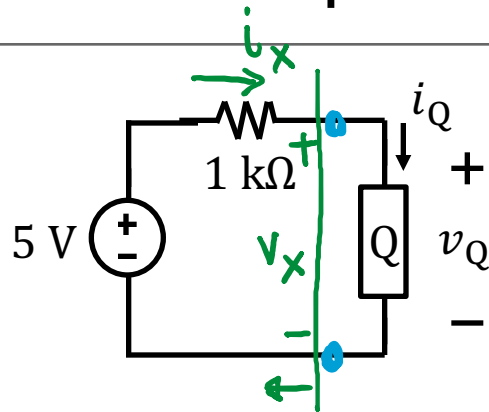Example 1: Graphical Analysis using Load Line




$$i_Q = \begin{cases} 0 & \text{if } v_Q < 1 \text{ V} \\ 0.5(v_Q - 1)^2 \text{ mA} & \text{if } v_Q \geq 1 \text{ V} \end{cases}$$

$$i_x = i_Q$$



$$v_x = v_Q$$

v_x vs. i_x

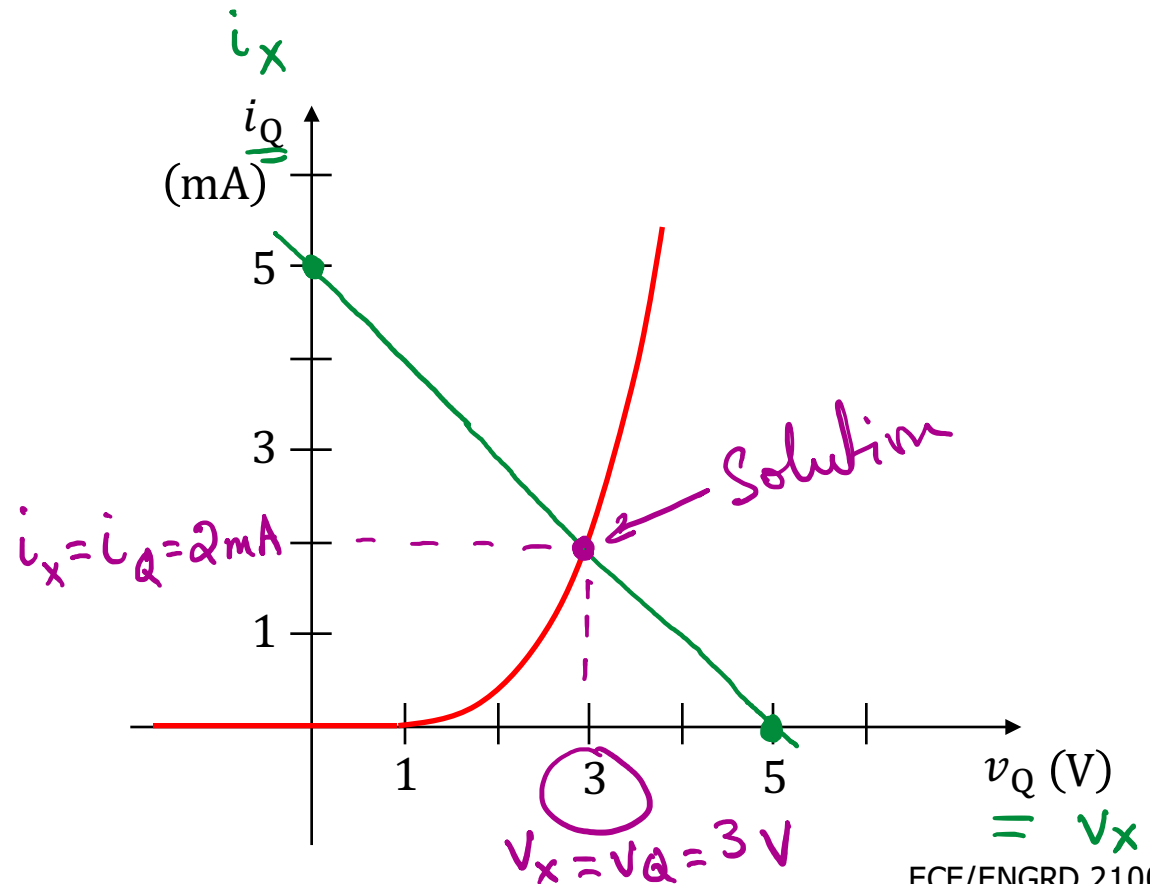
$$v_x = 5 \text{ V} - 1 \text{ k}\Omega (i_x)$$



Zener Diode

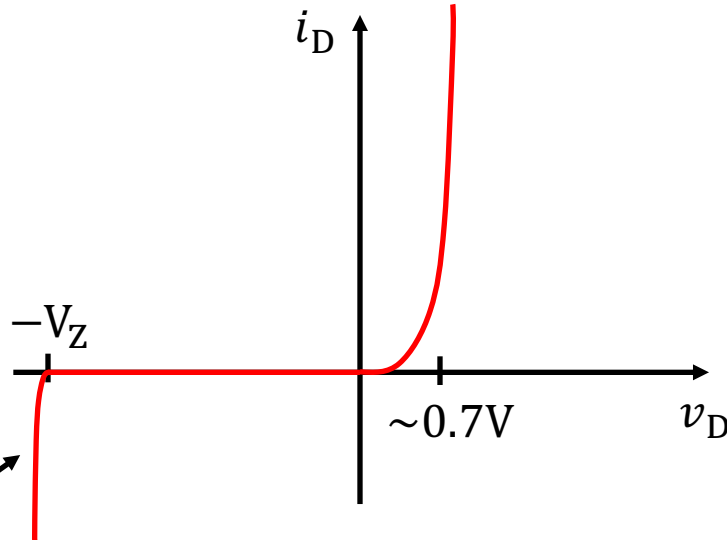
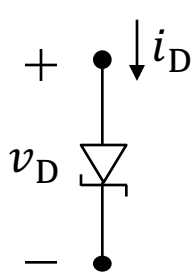


Engineered
Reverse
Breakdown

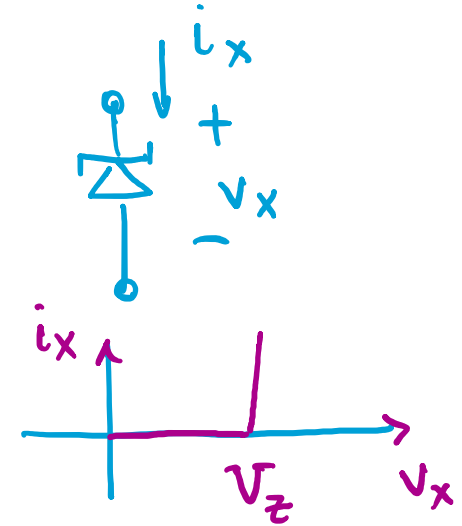

- Behaves mostly like a normal diode
- Reverse breakdown occurs typically with a sharper knee at designed voltage



Regulated Power Supply using Zener Diode

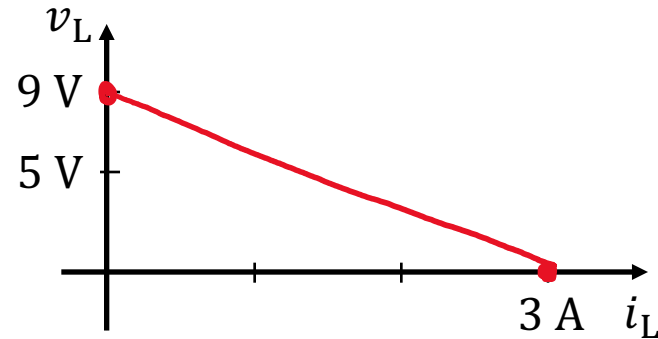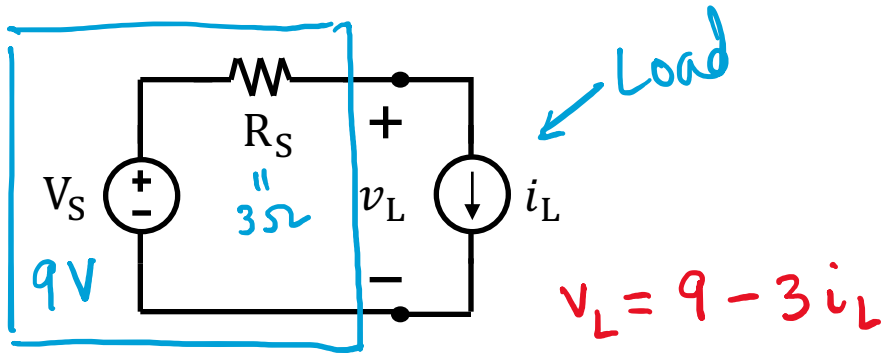


$V_S = 9\text{ V}$

$R_S = 3\ \Omega$

$V_Z = 5\text{ V}$

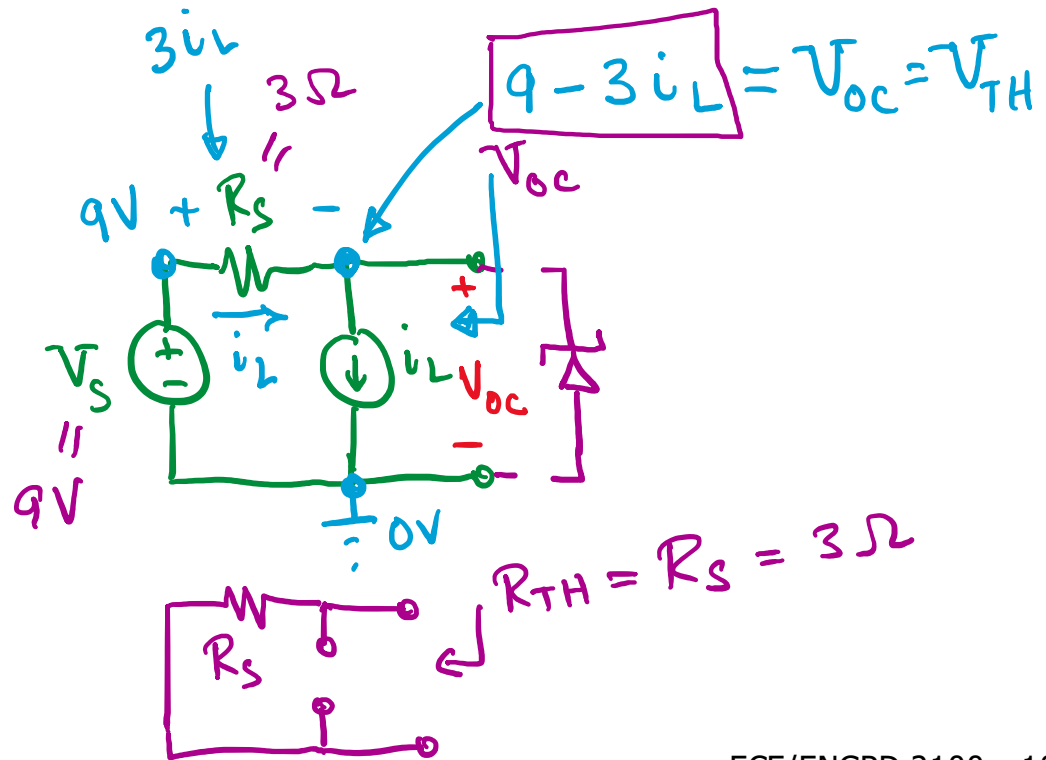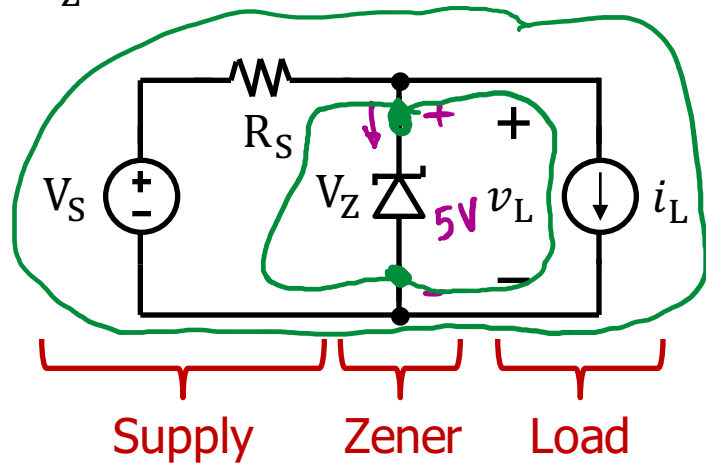

Regulated Power Supply (Cont.)


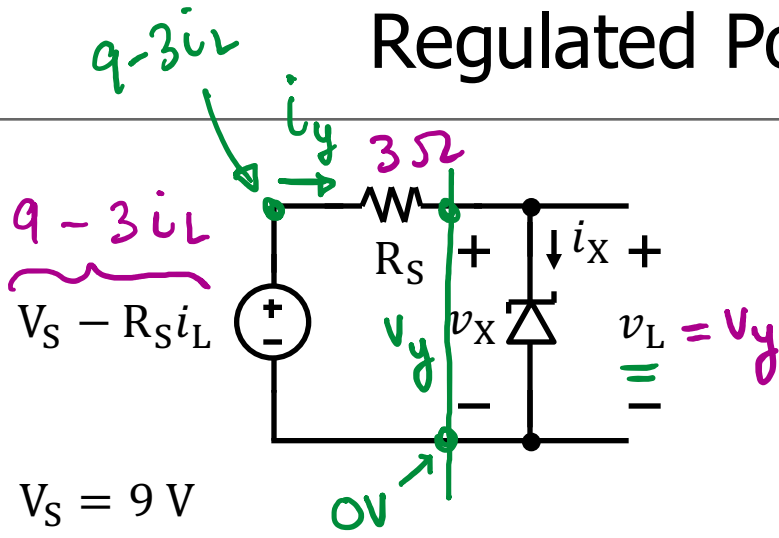


$$v_Y = (9 - 3i_L) - i_Y(3\ \Omega)$$




$$v_Y = 0 \Rightarrow i_Y = 3 - i_L$$

$$9 - 3i_L = 5$$
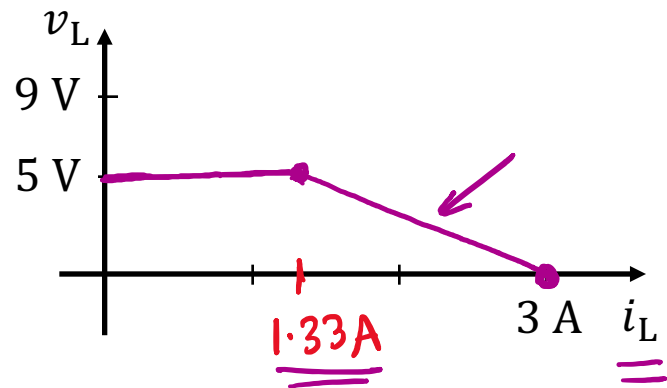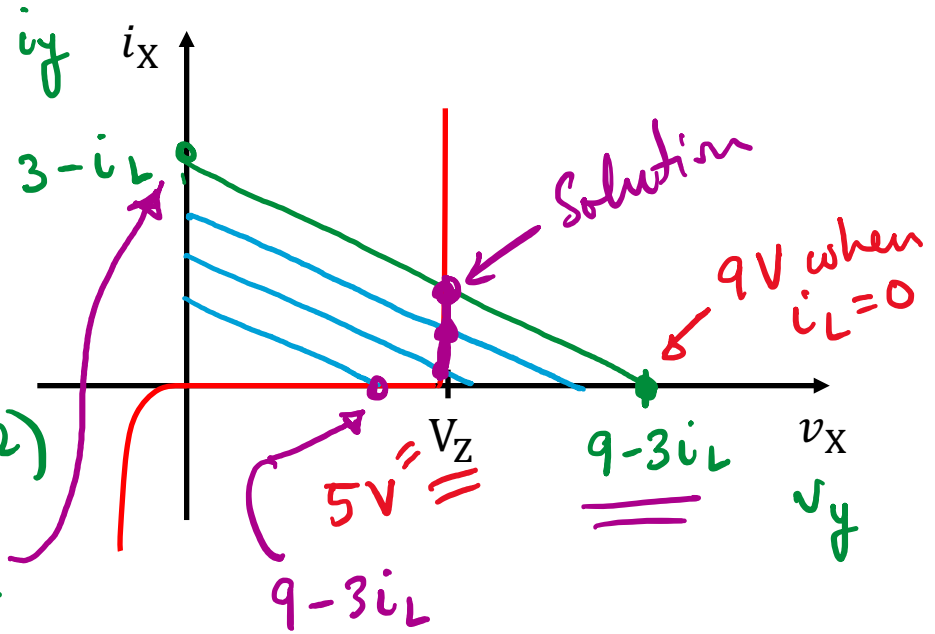
$$\Rightarrow 3i_L = 4 \Rightarrow i_L = 1.33\text{ A}$$



Piecewise Linear (Approximate) Analysis

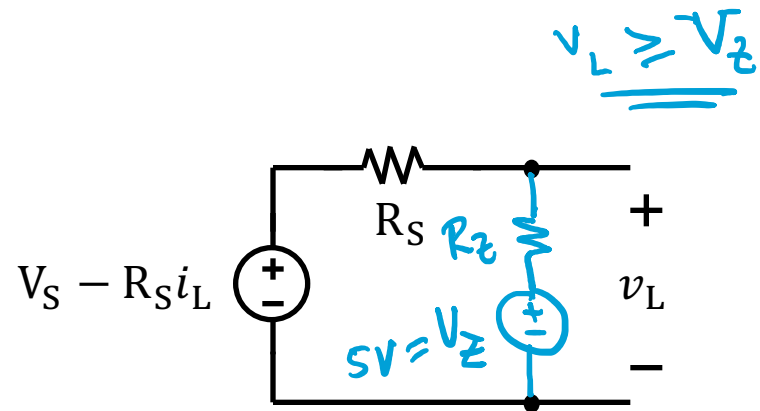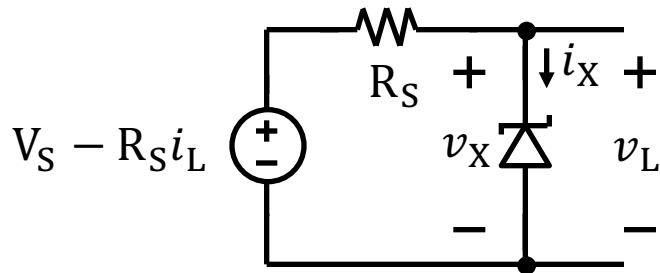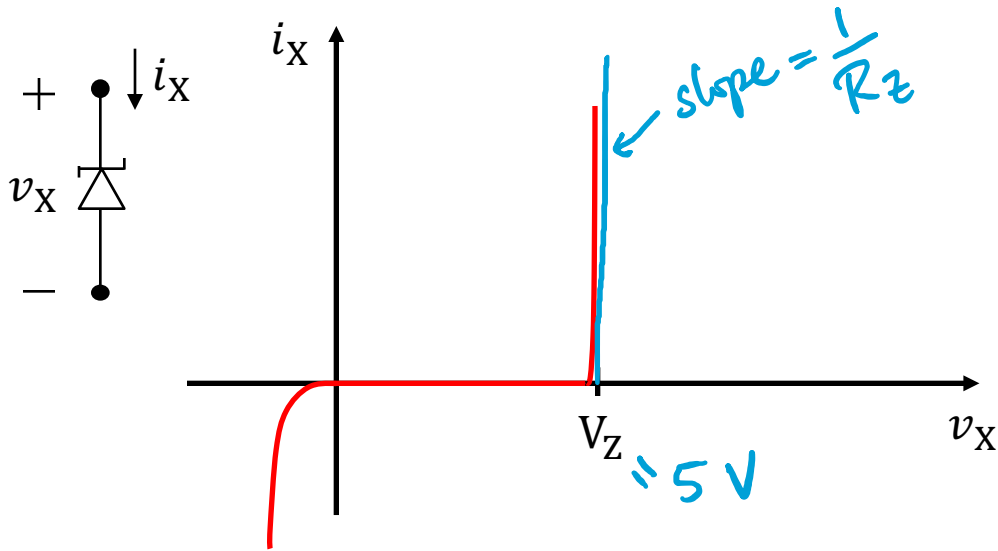

$$\underline{\underline{v_L \geq V_Z}}$$